

$$\text{Maximum power} = \frac{V^2}{2X_C} = \frac{100^2}{2 \times 1} = 5000 \text{ W}$$

16.10. R-L-C SERIES CIRCUIT

This is a general series a.c. circuit. Fig. 16.23 shows R , L and C connected in series across a supply voltage V (r.m.s.). The resulting circuit current is I (r.m.s.).

\therefore Voltage across R , $V_R = IR$... V_R is in phase with I

Voltage across L , $V_L = IX_L$... where V_L leads I by 90°

Voltage across C , $V_C = IX_C$... where V_C lags I by 90°

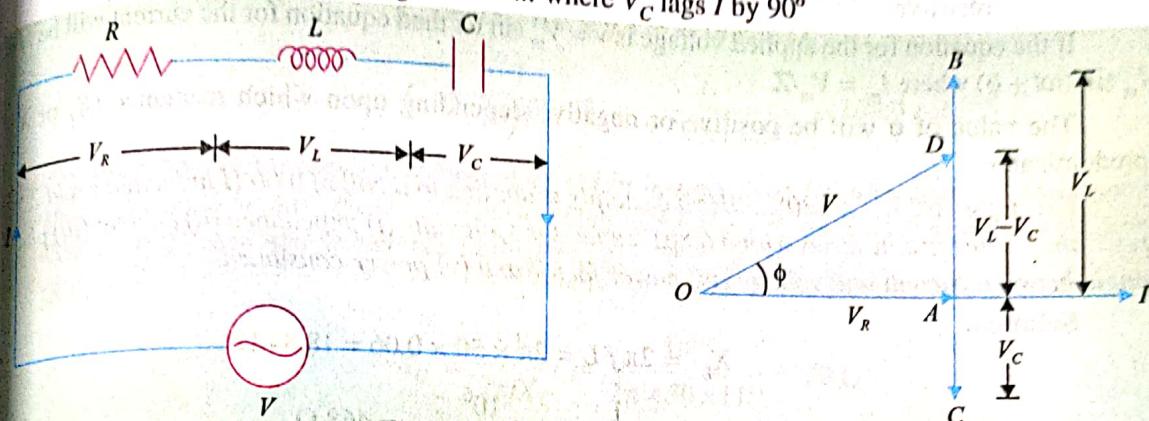


Fig. 16.23

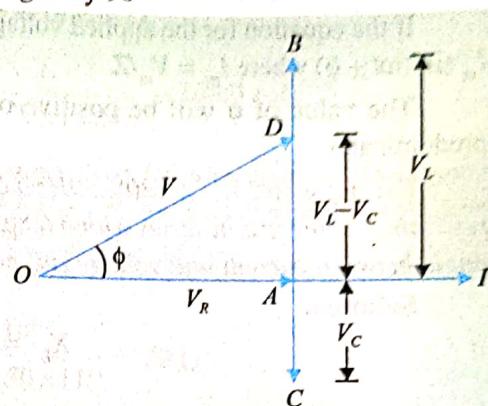


Fig. 16.24

As before, the phasor diagram is drawn taking current as the reference phasor. In the phasor diagram (See Fig. 16.24), OA represents V_R , AB represents V_L and AC represents V_C . It follows that the circuit can either be effectively inductive or capacitive depending upon which voltage drop (V_L or V_C) is predominant. For the case considered, $V_L > V_C$ so that net voltage drop across $L-C$ combination is $V_L - V_C$ and is represented by AD . Therefore, the applied voltage V is the phasor sum of V_R and $V_L - V_C$ and is represented by OD .

$$\begin{aligned} V &= \sqrt{V_R^2 + (V_L - V_C)^2} \\ &= \sqrt{(IR)^2 + (IX_L - IX_C)^2} = I\sqrt{R^2 + (X_L - X_C)^2} \end{aligned}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

The quantity $\sqrt{R^2 + (X_L - X_C)^2}$ offers opposition to current flow and is called **impedance** of the circuit.

$$\text{Circuit power factor, } \cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}} \quad \dots(i)$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R} \quad \dots(ii)$$

$$\text{Power consumed, } P = VI \cos \phi = *I^2 R$$

$$P = VI \cos \phi = (IZ) I \times \frac{R}{Z} = I^2 R$$

This is expected because there is no power loss in L or C .

Three cases of R-L-C series circuit. We have seen that the impedance of a *R-L-C* series circuit is given by :

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

- (i) When $X_L - X_C$ is positive (*i.e.* $X_L > X_C$), the phase angle ϕ is positive and the circuit is inductive.
- (ii) When $X_L - X_C$ is negative (*i.e.* $X_C > X_L$), the phase angle ϕ is negative and the circuit is capacitive.
- (iii) When $X_L - X_C$ is zero (*i.e.* $X_L = X_C$), the phase angle ϕ is zero and the circuit is purely resistive.

If the equation for the applied voltage is $v = V_m \sin \omega t$ then equation for the current will be : $i = I_m \sin(\omega t \pm \phi)$ where $I_m = V_m/Z$.

The value of ϕ will be positive or negative depending upon which reactance (X_L or X_C) predominates.

Example 16.24. A 230V, 50Hz *a.c.* supply is applied to a coil of 0.06 H inductance and 2.5Ω resistance connected in series with a 6.8μF capacitor. Calculate (i) impedance (ii) current (iii) phase angle between current and voltage (iv) power factor and (v) power consumed.

Solution.

$$X_L = 2\pi f L = 2\pi \times 50 \times 0.06 = 18.84 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{10^6}{2\pi \times 50 \times 6.8} = 468 \Omega$$

$X = X_L - X_C = 18.84 - 468 = -449.16 \Omega$
 (i) Impedance of the circuit $Z = \sqrt{R^2 + X^2} = \sqrt{(2.5)^2 + (-449.16)^2} = 449.2 \Omega$
 (ii) Current flowing in the circuit $I = V/Z = 230/449.2 = 0.512 \text{ A}$

$$(iii) \quad \phi = \tan^{-1} \frac{X}{R} = \tan^{-1} \frac{-449.16}{2.5} = -89.7^\circ$$

The negative sign with ϕ shows that current is leading the voltage.

$$(iv) \quad \text{p.f.} = \cos \phi = R/Z = 2.5/449.2 = 0.0056 \text{ lead}$$

$$(v) \quad P = VI \cos \phi = 230 \times 0.512 \times 0.0056 = 0.66 \text{ W}$$

Example 16.25. A resistance R , an inductance $L = 0.01H$ and a capacitance C are connected in series. When an alternating voltage $v = 400 \sin(3000t - 20^\circ)$ is applied to the series combination, the current flowing is $10\sqrt{2} \sin(3000t - 65^\circ)$. Find the values of R and C .

Solution.

$$\phi = 65^\circ - 20^\circ = 45^\circ \text{ lag i.e. circuit is inductive.}$$

$$X_L = \omega L = 3000 \times 0.01 = 30 \Omega$$

$$\tan 45^\circ = X/R \therefore X = R$$

$$Z = V_m/I_m = 400/10\sqrt{2} = 28.3 \Omega$$

$$Z^2 = R^2 + X^2 = R^2 + R^2 = 2R^2$$

$$R = Z/\sqrt{2} = 28.3/\sqrt{2} = 20 \Omega$$

$$X = X_L - X_C$$

$$X_C = X_L - X = 30 - 20 = 10 \Omega$$

Now

∴

$$C = \frac{1}{\omega X_C} = \frac{1}{3000 \times 10} = 33.3 \times 10^{-6} \text{ F}$$

Example 16.26. A coil of resistance 8Ω and inductance 0.03 H is connected to an a.c. supply $240 \text{ V}, 50 \text{ Hz}$. Calculate the value of capacitance which when connected in series with the above solution, causes no change in the value of current and power taken from the supply.

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.03 = 9.424 \Omega$$

To maintain the same current and power, the impedance of the circuit should not change. This is possible if the series capacitor has a capacitive reactance equal to twice the inductive reactance i.e.

$$X_C = 2X_L = 2 \times 9.424 = 18.848 \Omega$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 18.848} = 168.9 \times 10^{-6} \text{ F}$$

Example 16.27. A coil of p.f. 0.8 is connected in series with a $110 \mu\text{F}$ capacitor. The supply frequency is 50 Hz . The p.d. across the coil is found to be equal to the p.d. across the capacitor. Calculate the resistance and inductance of the coil.

Solution.

$$\text{Given } X_C = \frac{1}{2\pi f C} = \frac{10^6}{2\pi \times 50 \times 110} = 29 \Omega$$

Now

$$I Z_{\text{coil}} = IX_C$$

$$\therefore Z_{\text{coil}} = X_C = 29 \Omega$$

For the coil,

$$\cos \phi = R/Z_{\text{coil}}$$

$$\therefore R = Z_{\text{coil}} \cos \phi = 29 \times 0.8 = 23.2 \Omega$$

$$\text{Reactance of coil, } X_L = Z_{\text{coil}} \sin \phi = 29 \times 0.6 = 17.4 \Omega$$

$$\therefore L = \frac{X_L}{2\pi f} = \frac{17.4}{2\pi \times 50} = 0.055 \text{ H}$$

Example 16.28. A resistance of 1 ohm , an inductance of 1 henry and a capacitance of 1 farad are connected in series across a voltage and the line current is 1 A . Find the energy consumed in one hour.

Solution. Energy is only consumed in R since L or C does not consume any energy.

$$\text{Energy consumed} = I^2 Rt = (1)^2 \times 1 \times 3600 = 3600 \text{ J}$$

TUTORIAL PROBLEMS

- A circuit is made up of 5Ω resistance, 0.2 H inductance and $60 \mu\text{F}$ capacitance in series. If the circuit current is 20 A at a supply frequency of 50 Hz , find the applied voltage. [219 V]
- A series circuit consists of a non-inductive resistor of 10Ω , an inductor having a reactance of 50Ω and a capacitor having a reactance of 30Ω . It is connected to a 230 V a.c. supply. Calculate (i) current (ii) the power consumed and (iii) the power factor. [(i) 10.3 A (ii) 1060 W (iii) 0.447 lag]
- A coil of resistance 20Ω is in series with an inductance of 0.04 H . A supply of 230 V , 50 Hz is applied to the combination. Determine the capacitance which when connected in series with the coil causes no change in the magnitude and power taken from the supply. [$67.5 \mu\text{F}$]