

10 August 23

22 August 2023 22:13

## # Positional Weight method [Converting any type to decimal]

$$(37)_{10} = ( \quad )_{10}$$

Weight according to the position

$$\begin{aligned} &\Rightarrow 3 \times 8^0 + 7 \times 8^0 \\ &= 3 \times 8 + 7 \\ &= 24 + 7 \\ &= \boxed{31} \end{aligned}$$

$$[1A]_{16} = ( \quad )_{10}$$

$$\begin{aligned} &= 1 \times 16^1 + 10 \times 16^0 \\ &= 16 + 10 = \boxed{26} \end{aligned}$$

$$[100]_2 = [ \quad ]_{10}$$

$$\begin{aligned} &= 1 \times 2^2 + 0 \times 2^1 + 0 \times 2^0 \\ &= \boxed{4} \end{aligned}$$

$$(23.5)_{10} = ( \quad )_2$$

$$\begin{array}{r} 2 | 23 \\ 2 | 11 \quad 1 \\ 2 | 5 \quad 1 \\ 2 | 2 \quad 1 \\ 2 | 1 \quad 0 \\ \hline & 1 \end{array}$$

$$(10111.1)_2$$

$$\begin{aligned} 0.5 \times 2 &= \boxed{1.0} \\ 0 \times 2 &= 0 \end{aligned}$$

for

$$(23.6)_{10} = (10111.1001)_2$$


$$\begin{aligned} 0.6 \times 2 &= \boxed{1.2} \\ 0.2 \times 2 &= \boxed{0.4} \\ 0.4 \times 2 &= \boxed{0.8} \\ 0.8 \times 2 &= \boxed{1.6} \\ 0.6 \times 2 &= \boxed{1.2} \end{aligned}$$

For converting from Hexadecimal (16) to Octal (8)

e.g.  $[\underline{\text{CAFE}}]_{16} = [ \quad ]_8$

for converting from Hexadecimal (16) to Octal (8)

e.g.  $[CAFE]_{16} = [ ]_8$

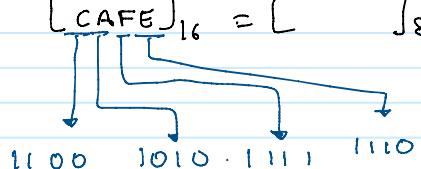


$$= \frac{C}{1100} \frac{A}{1010} \frac{F}{1111} \frac{E}{1110}$$

↓  
Converting to octal

$$\begin{array}{r} 001 \ 100 \ 101 \ 011 \ 111 \ 110 \\ \hline 1 \quad 4 \quad 5 \quad 3 \quad 7 \quad 6 \end{array}$$

$$= (145376)$$

Converting it back to hexadecimal

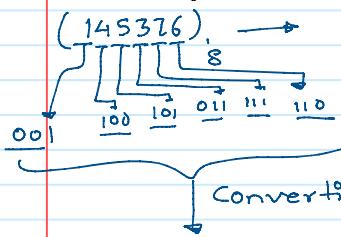

↓  
Converting to Hexadecimal

$$\begin{array}{r} 1100 \ 1010 \ 1111 \ 1110 \\ \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \\ C \quad A \quad F \quad E \end{array}$$

$$[CAFE]_{16}$$

## \* Complement

Q. Find 1's complement for '0110'

Ans:-

$$\begin{array}{r} 1 \ 1 \ 1 \ 1 \\ - 0 \ 1 \ 1 \ 0 \\ \hline 1 \ 0 \ 0 \ 1 \end{array}$$

complement is applicable only for negative numbers

Q. Find 2's complement for '(0110)<sub>2</sub>'

Ans:- 1's complement of 0110

$$\begin{array}{r} 1111 \\ - 0110 \\ \hline 1001 \\ + 1 \\ \hline 1010 \end{array}$$

Q. For a number  $(1110)_2$ , find 2's complement.

Ans:-

$$\begin{array}{r}
 & | & | & | & | \\
 - & 1 & 1 & 1 & 0 \\
 \hline
 + & 0 & 0 & 0 & 1 \\
 \hline
 & 0 & 0 & 1 & 0
 \end{array} \rightarrow 1\text{'s complement}$$

$$\begin{array}{r}
 & | & | & | & | \\
 - & 1 & 1 & 1 & 0 \\
 \hline
 + & 0 & 0 & 1 & 0 \\
 \hline
 & 0 & 0 & 1 & 0
 \end{array} \rightarrow 2\text{'s complement}$$

Q. For a large number like  $(11011100111)_2$   
Find 2's complement.

Ans:- First find '1' from right,

$\begin{array}{r}
 & | & | & 0 & 1 & 1 & 1 & 0 & 0 & 1 & 1
 \end{array}$ 
  
 So, now just keep '1' from the very right position 1 and take the complement of remaining numbers.

$$\begin{array}{r}
 & | & | & | & | & | & | & | & | & | \\
 - & 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \\
 \hline
 & 1 & 1 & 0 & 1 & 1 & 0 & 0 & 1 & 1
 \end{array} \rightarrow$$

$$\begin{array}{r}
 & | & | & | & | & | & | & | & | & | \\
 - & 1 & 1 & 0 & 1 & 1 & 0 & 0 & 1 & 1 \\
 \hline
 & 0 & 0 & 1 & 0 & 0 & 1 & 1 & 0 & 0
 \end{array}$$

Q. For  $(12345)_{10}$ , find 10's complement

Ans:-

9's complement:-

$$\begin{array}{r}
 & 9 & 9 & 9 & 9 & 9 \\
 - & 1 & 2 & 3 & 4 & 5 \\
 \hline
 & 8 & 7 & 6 & 5 & 4
 \end{array}$$

$$\begin{array}{r}
 10\text{'s complement} \\
 = 87654 \\
 + 1 \\
 \hline
 87655
 \end{array}$$

If the base  $[C \neq 10]$  is even, take the previous complement.

If the base is odd take the same number for complement.

Q. For  $(12346)_7$  Find 8's complement.

$$\begin{array}{r}
 7\text{'s complement} = \\
 - 7 & 7 & 7 & 7 & 7 \\
 - 1 & 2 & 3 & 4 & 6 \\
 \hline
 6 & 5 & 4 & 3 & 1
 \end{array}$$

$$\begin{array}{r}
 8\text{'s complement} = \\
 - 6 & 5 & 4 & 3 & 2 \\
 + 1 \\
 \hline
 \end{array}$$

Q. Add

$$\begin{array}{r}
 & | & | & | & | & | \\
 - & 1 & 1 & 0 & 1 & 1 \\
 \hline
 + & 1 & 1 & 0 & 1 & 0 1 \\
 \hline
 & 1 & 1 & 0 & 1 & 1 0 0
 \end{array}$$

Q. Subtract using 1's complement

$$\begin{array}{r}
 - & 0 & 1 & 1 & 0 \\
 \underline{-} & 1 & 1 & 1 & 0 \\
 \text{6} & & & & \\
 -14 & \xrightarrow{\text{(-8)}} & \text{should be the answer}
 \end{array}$$

Since while subtracting, it has become a negative number.

By taking complement of it and adding it we get

$$\begin{array}{r}
 + & 0 & 1 & 1 & 0 \\
 + & 0 & 0 & 0 & 1 \\
 - & [0 & 1 & 1 & 1]
 \end{array}$$

No extra digit

Since the number is negative, take its complement.

If we get some extra digits, it implies the answer is positive or else the answer is negative.

[1 0 0 0]  $\rightarrow$  (-8) we are correct.

e.g.

$$\begin{array}{r}
 1 & 1 & 1 & 0 \\
 - 0 & 1 & 1 & 0
 \end{array}
 \xrightarrow{\quad}
 \begin{array}{r}
 + & 1 & 1 & 1 & 0 \\
 + & 1 & 0 & 0 & 1 \\
 \hline
 1 & 0 & 1 & 1 & 1
 \end{array}$$

extra digit

isko yaha rakhe add karo

$$\begin{array}{r}
 1 & 0 & 0 & 0 \\
 \hline
 +8
 \end{array}$$

# Sign-Bit Representation:-

unsigned numbers are positive numbers, having no space for negative numbers.

e.g. Express numbers in unsigned but 4-bit format.

$$\begin{array}{l}
 0 \longrightarrow 0 0 0 0 \\
 1 \longrightarrow 0 0 0 1 \\
 \vdots \\
 7 \longrightarrow 0 1 1 1
 \end{array}$$

Sign bit is used to represent the sign of a number, '1' bit is reserved in signed bit representation.

e.g.

0 →	0 0 0
1 →	0 0 1
2 →	0 1 0
3 →	0 1 1
4 →	1 0 0
5 →	1 0 1
6 →	1 1 0
7 →	1 1 1

this bit represent  
+ve sign.

0 →	1 0 0
-1 →	1 0 1
-2 →	1 1 0
-3 →	1 1 1
-4 →	1 0 0
-5 →	1 0 1
-6 →	1 1 0
-7 →	1 1 1

this bit represents  
-ve sign

16-August-23

e.g. Here are some 4-bit representations:-

Sign-bit representation	1's complement form
0 0 0 0	+0
0 0 0 1	+1
0 0 1 0	+2
0 0 1 1	+3
0 1 0 0	+4
0 1 0 1	+5
0 1 1 0	+6
0 1 1 1	+7
1 0 0 0	-0
1 0 0 1	-1
1 0 1 0	-2
1 0 1 1	-3
1 1 0 0	-4
1 1 0 1	-5
1 1 1 0	-6
1 1 1 1	-7

This bit is reserved for sign  
Taking complement of these three bit.

2's complement	
0 0 0 0	+0
0 0 0 1	+1
0 0 1 0	+2
0 0 1 1	+3
0 1 0 0	+4
0 1 0 1	+5
0 1 1 0	+6
0 1 1 1	+7
1 0 0 0	-8
1 0 0 1	-7
1 0 1 0	-6
1 0 1 1	-5
1 1 0 0	-4
1 1 0 1	-3
1 1 1 0	-2
1 1 1 1	-1

for 2's complement of,

$$\begin{array}{r} 0 \ 0 \ 0 \\ \swarrow +1 \\ 1 \ 1 \ 1 \end{array} \rightarrow [1\text{'s complement}]$$

$$\begin{array}{r} 1 \ 0 \ 0 \ 0 \\ \swarrow +1 \\ 1 \ 0 \ 0 \ 1 \end{array} \rightarrow [2\text{'s complement}]$$


$$= 8$$

for 2's complement of a representation, whose unit's place has 1.

0 1 1 → keep the '1' on the right-most end, take the complement of remaining bit.

→ for 0 1 1, 2's complement
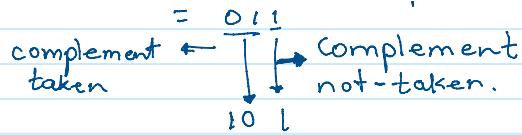
$$\begin{array}{r} 0 \ 1 \ 1 \\ \swarrow \text{complement taken} \quad \swarrow \text{complement not-taken.} \end{array}$$



For a 4-bit representation, the formula for finding the range of sign-bit form is,

-  $[2^{n-1} - 1]$  to  $[2^{n-1} - 1]$  → this is also applicable for 1's complement form.

For 2's complement form,

-  $[2^{n-1}]$  to  $[2^{n-1} - 1]$

e.g. For a 3-bit binary value, Find the range of 1's complement form, and 2's complement

→ for 1's complement,

-  $[2^{(3-1)} - 1]$  to  $[2^{(3-1)} - 1]$

= -[3] to [3]

for 2's complement,

-  $[2^{(3-1)}]$  to  $[2^{(3-1)} - 1]$

-[4] to [3].

17-August-23

\* Addition through 1's sign-bit form:- [5-bit available]

$$\begin{array}{r} + -3 \\ + 6 \\ + 3 \end{array} \quad \begin{array}{r} 11100 \\ 00110 \\ \hline 100010 \end{array}$$

↓  
Extra ⇒ positive number.  
digit

$$\begin{array}{r} 100010 \\ \hline 00011 \end{array}$$

↓  
+ 3

$$\begin{array}{r} 3 \\ - 6 \end{array} \quad \begin{array}{r} 00011 \\ 11001 \\ \hline 11100 \end{array}$$

↓  
No Extra = -ve sign

} Since the answer is negative, take complement  
= -6

$$\begin{array}{r} -9 \\ \hline 10110 \end{array}$$

$9 = \begin{array}{r} 1001 \\ 0110 \end{array}$

e.g.

$$\begin{array}{r}
 -9 \rightarrow +101110 \\
 -9 \rightarrow \underline{101110} \\
 \hline
 +13 \quad \downarrow \\
 \underline{\underline{101100}}
 \end{array}$$

positive number

$$q = \begin{matrix} 1 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 \end{matrix}$$

$$\begin{array}{r}
 \textcircled{1} 01100 \\
 +1 \quad \downarrow \\
 \hline
 01101
 \end{array}$$

$\downarrow$   
 $+13$

The answer is wrong because the range of 5-bit representation is from -15 to 15.

Now, solving it by making it a 6 bit numbers.

$$\begin{array}{r}
 -9 \quad 110110 \\
 -9 \quad \underline{110110} \\
 \hline
 +1 \quad \textcircled{1} 101100 \\
 \text{Extra digit} \quad \text{→} \\
 \text{→} \quad \textcircled{1} 01101 \\
 \text{-ve} \quad \downarrow \text{taking complement} \\
 \hline
 10010 \\
 \downarrow \\
 -18
 \end{array}$$

### \* Addition through 2's sign bit form [5-bit available]

$$\begin{array}{r}
 -3 \rightarrow 11101 \\
 +6 \rightarrow 00110 \\
 \hline
 +3 \quad \text{Just ignore it} \\
 \text{→} \quad \text{+ve sign} \\
 \text{→} \quad \text{+3} \\
 \hline
 \text{→} \quad \text{answer positive}
 \end{array}$$

$$\begin{array}{r}
 -6 \rightarrow +11010 \\
 +3 \rightarrow 00011 \\
 \hline
 -3 \quad \text{→ -ve sign} \\
 \text{→ Since, negative. Take complement} \\
 \text{→ 0011} \\
 \downarrow \\
 -3
 \end{array}$$

# BCD Code [Binary coded decimal] :-  
It is a 4-bit representation only

Decimal

0	0 0 0 0	]
1	0 0 0 1	
2	0 0 1 0	

0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1

Valid only. } From 10-15  
it is all invalid state.

e.g. For  $(12)_{10}$ , What is the BCD code?

$$= (0001 \ 0010)_{BCD}$$

\* Self- Complementary Code :-

\* BCD addition.

e.g.

$\frac{9}{+3}$	$+ 1001 \longrightarrow$ Valid BCD state
$\underline{12}$	$0011 \longrightarrow$ Valid BCD state
	$1100 \longrightarrow$ Invalid BCD state
$0000 \ 0 + 0110 \ \downarrow$	we will add +6 in the invalid state to get the code
$\underline{\underline{0010}}$	↓
↓	↓
1	2

$(\underline{\underline{00010010}})$  A valid BCD state

e.g.

$\frac{28}{+32}$	$+ 0010 \nearrow$ valid	$1000 \longrightarrow$ valid
$\underline{60}$	$0011 \nearrow$ valid	$0010 \longrightarrow$ valid
	$0101$	$1010$
	$\underline{\underline{0110}}$	$\underline{\underline{0000}}$
6	0.	

$= 60.$

e.g.

$\frac{239}{+148}$	$+ 0010 \nearrow$	$0011 \nearrow$	$1001 \nearrow$	$1000 \nearrow$
$\underline{387}$	$0001$	$0100$	$1000$	$1000$
	$\underline{\underline{0011}}$	$\underline{\underline{1000}}$	$\underline{\underline{0000}}$	$\underline{\underline{0000}}$
3	8	$\underline{\underline{0110}}$	$\underline{\underline{0111}}$	

Valid state

Is group se  
carry forward true hai,  
to them +6 (0110)

$$\begin{array}{r}
 & \overbrace{\phantom{0}}^{\text{carry}} & \overbrace{8}^{\text{forward sum hai}}, \\
 3 & + 0 & 1 & 1 & 0 \\
 & \overbrace{0 & 1 & 1 & 1}^{\text{to ham +6(0110)}} \\
 & & \overbrace{7}^{\text{add korenge.}}
 \end{array}$$

- | carry  
forward true tail,  
to them +6 (0110)  
add carriage.

## \* BCD Subtraction:-

e.g.

$$\begin{array}{r}
 23 \\
 + 0010 \\
 \hline
 12 \\
 \hline
 11
 \end{array}
 \quad
 \begin{array}{r}
 0011 \\
 + 0010 \\
 \hline
 0001 \\
 \hline
 0001
 \end{array}$$

$$\begin{array}{r} \text{for } \\ \begin{array}{r} -1 & +10 \\ 1 & 2 \\ \hline -3 & -3 \end{array} \end{array}$$


Similarly, for  
binary number  
system,

$$\begin{array}{r} [1-1=0] \xleftarrow{-1} x \cancel{\times} \xrightarrow{+2} [2+0=2] \\ \hline - & 1 \\ 0 & 1 \end{array}$$
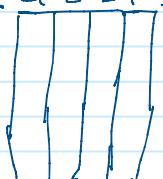
## **★ Self - Complementary Code :-**

The code, whose sum of values of weight is 9 is called self-complementary code.

$$\text{e.g. } \frac{4\ 2\ 2\ 1}{\boxed{\phantom{0}}\ \boxed{\phantom{0}}\ \boxed{\phantom{0}}\ \boxed{\phantom{0}}} = 4+2+2+1 = 9.$$



	2	4	2	1	-
0 →	0	0	0	0	
1	0	0	0	1	
2	0	0	1	0	/
3	0	0	1	1	/
4	0	1	0	0	/
5	0	1	0	1	/
6	0	1	1	0	/
7	0	1	1	1	/
8	1	1	1	0	
9	1	1	1	1	

\* Lower Precedence Logic →

for '2', there are two possible  
Self-Complementary code in this '2421' format

$$0010 / \underline{\underline{1000}}$$

error ①  $\rightarrow$  MSB is used for lower number

now, '2' complement is 7, whose code is -

$$\begin{array}{r} 0 \ 1 \ 1 \ 1 \\ \hline \downarrow \end{array} / \begin{array}{r} 1 \ 1 \ 0 \ 1 \end{array}$$

Now, 2's complement is 1, whose code is -  

$$\begin{array}{r} 0 \ 1 \ 1 \ 1 \ / \\ \downarrow \\ \text{complement} \\ \text{of } 1000 \end{array}$$

LSB is used representing higher value.

This is not correct. So, for '2'  $0010$  is more genuine.

6    4    1    -2

Is it also a self-complementary code?

Homework.

### # Excess-3 Code:-

{range  $\rightarrow 3-12$ }

$BCD+3 = \text{Excess-3 code}$  {This code does not have weight}  
 {This code is self-complementary code}

$$0\ 0\ 0\ 0 = 0\ 0\ 1\ 1$$

$$0\ 0\ 0\ 1 = 0\ 1\ 0\ 0$$

$$0\ 0\ 1\ 0 = 0\ 1\ 0\ 1$$

$$0\ 0\ 1\ 1 = 0\ 1\ 1\ 0$$

$$0\ 1\ 0\ 0 = 0\ 1\ 1\ 1$$

$$0\ 1\ 0\ 1 = 1\ 0\ 0\ 0$$

$$0\ 1\ 1\ 0 = 1\ 0\ 0\ 1$$

$$0\ 1\ 1\ 1 = 1\ 0\ 1\ 0$$

$$1\ 0\ 0\ 0 = 1\ 0\ 1\ 1$$

$$1\ 0\ 0\ 1 = 1\ 1\ 0\ 0$$


$$\text{e.g. } (123)_{10} = (\quad)_{5n-3}$$

$$= (\underline{\quad} \underline{\quad} \underline{\quad})_{5n-3}$$

### # Gray Code:-

{Mirror Image Code} {Cyclic Code}

e.g.

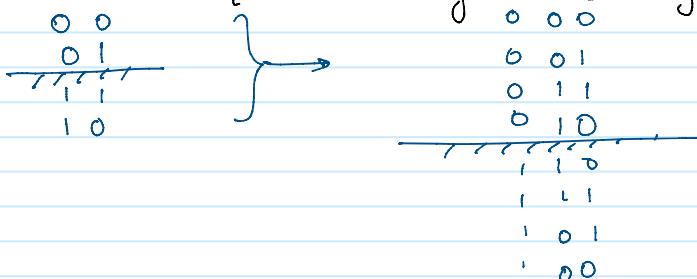

For XOR Gate,

jaha bhi odd

number of 1

hoga waha

output 1 hoga.


0	0	0
0	1	1
1	0	1
1	1	0

R . L . + 1 R 0 1 1 1 1 . No. of


hoga awha  
output 1 hoga.

For Gray code, fix the leftmost digit  
and in the right digit just write the  
output of XOR Gates.

e.g.

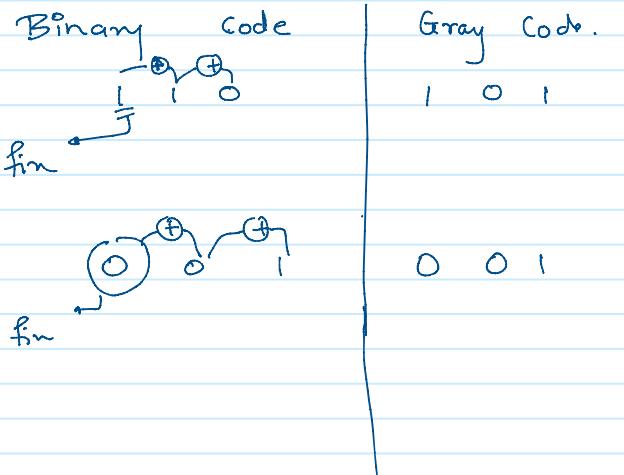
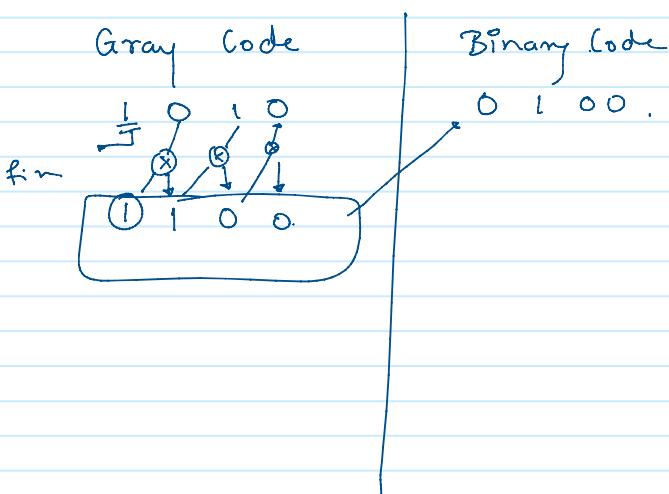
# Conversion of Gray Code to Binary,  
for this conversion go angle-wise.



# Logic Gates:-

AND

0	0	$\rightarrow$	0
0	1	$\rightarrow$	0
1	0	$\rightarrow$	0
1	1	$\rightarrow$	1

OR

0	0	$\rightarrow$	0
0	1	$\rightarrow$	1
1	0	$\rightarrow$	1
1	1	$\rightarrow$	1

Digital Language main OR  $\rightarrow$  Addition.  
AND  $\rightarrow$  Multiplication.

\* Commutative Law:-

$A+B = B+A$	$A+(B+C) = (A+B)+C$
$A \cdot B = B \cdot A$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$

\* Distributive Law:-

$$A \cdot (B+C) = A \cdot B + A \cdot C$$

\*  $A \cdot A = A$       \*  $A+A = A$   
 $A \cdot \bar{A} = 0$        $A+\bar{A} = 1$   
 $A \cdot 1 = A$        $A+1 = 1$   
 $A \cdot 0 = 0$        $A+0 = A$

\* De Morgan's Law:-

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

\*  $\underbrace{1+n+y+z+yz+yzz=1}$

as  $n, y, z$  may be 0 or 1  
in binary.

# Transposition Theorem:-

\*  $[A+B][A+C] \rightarrow (\underbrace{n+y+wz}_A)$   
 $= \underbrace{A \cdot A}_1 + A \cdot C + A \cdot B + B \cdot C$   
 $= A \underbrace{(1+C+B)}_1 + BC$   
 $= A + BC$

\*  $f = A\bar{B} + A\bar{B}\bar{C} + A\bar{B}\bar{C}D$   
 $= A(\bar{B} + \bar{B}\bar{C}) + A\bar{B}\bar{C}D$   
 $= A[(\bar{B} + B)(\bar{B} + \bar{C})] + A\bar{B}\bar{C}D$   
 $= A(\bar{B} + \bar{C}) + A\bar{B}\bar{C}D$   
 $= A\bar{B} + A\bar{C} + A\bar{B}\bar{C}D$   
 $= A\bar{B}(1 + \bar{C}D) + A\bar{C}$   
 $= A\bar{B} + A\bar{C}$   
 $= A(\bar{B} + \bar{C})$   
 $= A\bar{B}\bar{C}$

\*  $f = (n+y+z)(n+y+\bar{z}) + (n+\bar{y}z)$   
 $= (n+y+z\bar{z}) + (n+\bar{y})(n+z)$   
 $= \underbrace{(n+y)}_a + \underbrace{(n+\bar{y})}_{b'}(n+z)$   
 $= (n+y + n + \bar{y}) (n + \bar{y} + n + z)$   
 $= (1) (n+y+z)$   
 $= (n+y+z)$

\* Concensus Theorem :-

$$f = \overline{AB} + BC + \overline{A}C$$

$\Downarrow$   
 $\times$   
 $\Downarrow$

$$= [AB + \overline{A}C] \checkmark$$

\*  $f = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$

$$\begin{aligned} &= \overline{A}(\overline{B}C + B\overline{C}) + A(\overline{B}\overline{C} + BC) \\ &= \overline{A}(B \oplus C) + A(B \odot C) \\ &\quad \text{XOR Gate} \quad \text{XNOR Gate} \\ &B \oplus C = (\overline{B}C + B\overline{C}) \quad B \odot C = (\overline{B}\overline{C} + BC) \end{aligned}$$

$$= \overline{A}(y) + A(\bar{y})$$

$$= A \cdot \oplus y$$

$f = A \oplus B \oplus C$

A	B	f
0	0	0
0	1	1
1	0	1
1	1	0

SOP =  $\underbrace{AB}_{\text{True}} + A\overline{B} + \overline{A}B$  [Preferred NAND Gate]

True Logic

POS =  $[A+B]$  [Preferred NOR Gate]

False Logic

Q.  $f = A + c[\overline{AB} + \overline{BC}]$

Soln:-

$$\begin{aligned} &= A + c[\overline{A}\overline{B} \cdot \overline{B}\overline{C}] \\ &= A + c[(\overline{A}+\overline{B}) \cdot (\overline{B}+\overline{C})] \\ &= A + c[\overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B} + \overline{B}\overline{C}] \\ &= A + \overline{A}\overline{B}c + \overline{A}C + \overline{B}C + \overline{B} \\ &\quad \text{↓} \\ &= A + \overline{A}C(B+1) + \overline{B}C \\ &= A + \overline{A}C + \overline{B}C \\ &= A + c(\overline{A} + \overline{B}) \\ &= A + c(\overline{A} \cdot \overline{B}) \end{aligned}$$

# SOP [True Logic]

	a	b	f
i	0	0	0
ii	0	1	1 → True
iii	1	0	0
iv	1	1	1 → True

for ii,

$$\begin{array}{c} 0 \\ \downarrow \\ \bar{a} \end{array} \quad \begin{array}{c} 1 \\ \downarrow \\ b \end{array}$$

} For SOP,

$$\frac{\bar{a}b + ab}{\cancel{1}} = 1$$

in product form  
bolte hai!

from ii from iv

# POS:- [False Logic]

for i and iii;

$$f_{pos} = (\bar{a}+b)(\bar{a}+b)$$

inko literals in  
sum form bolte  
hai

$$\begin{array}{c} \bar{a} \\ \downarrow \\ 0 \end{array} \quad \begin{array}{c} b \\ \downarrow \\ 0 \end{array} \quad \begin{array}{c} \bar{a} \\ \downarrow \\ 1 \end{array} \quad \begin{array}{c} b \\ \downarrow \\ 0 \end{array}$$

from i from iii

$$\begin{aligned} &= \bar{a}\bar{a} + \bar{a}b + \bar{a}b + b \\ &= b(1 + \bar{a} + \bar{a}) \\ &= b \end{aligned}$$

a	b	c	
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned} f_{sop} &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + a\bar{b}\bar{c} + a\bar{b}c + abc \\ &= \bar{a} + \bar{b} + \bar{c} \end{aligned}$$

$$f_{pos} = \bar{a} + \bar{b} + \bar{c}$$

$$f_{sop} = f_{pos}$$

a	b	$f_{sop}$	→ min terms
0	0	1	
0	1	1	
1	0	1	
1	1	1	

a	b	$f_{SOP}$	→ min terms
0	0	→ 1	
0	1	→ 1	
1	0	→ 1	
1	1	→ 1	

Sum of all the literals in SOP is always 1.

Product of all the literals in POS is always 0.

$$f_{POS} = \underbrace{(a+b)}_{{\text{OR Gate}}} \overline{\underbrace{b+c}}_{{\text{AND Gate}}}$$

$$f_{SOP} = \underbrace{\overline{ab}}_{{\text{AND Gate}}} + \underbrace{bc}_{{\text{OR Gate}}}$$

AND OR = NAND NAND

OR AND = NOR NOR

			min terms	max terms
<u>a</u>	<u>b</u>	<u>c</u>	$\overline{ab\bar{c}}$	$(a+\bar{b}+c)$
0	1	0	→	
1	1	0	→ $ab\bar{c}$	$(\bar{a}+\bar{b}+c)$

$$f_{SOP} = [\overbrace{\overline{ab\bar{c}}}^{\text{Literals}} + \overbrace{\overline{ab\bar{c}}}^{\text{Literals}}] \rightarrow \text{SOP}$$

$$f_{POS} = [(a+b+c) \cdot (\bar{a}+\bar{b}+c)]$$

e.g.  $f = ab + bc \rightarrow$  [A SOP expression]

\* There are two universal gates

- a) NAND,
- b) NOR } Every gate can be designed using these

\* For SOP Logic, AND-OR Logic gate is preferred  
 $\text{AND - OR} = \text{NAND - NAND}$

\* For POS Logic, OR-AND Logic gate is preferred  
 $\text{OR-AND} = \text{NOR - NOR}$ .

Bubbled OR = NAND

Bubbled AND = NOR

## # Karnaugh Map [K-Map]

a	b	It Gives Gray Code		
		0\0	0\1	1\1
0	0			
0	1			
1	0			
1	1			

a	b	c		$a'bc$	00	01	11	10
0	0	0		0	0	1	3	2
1	1	1		1	4	5	7	6

# Rules :-

$$\begin{array}{l} a'b \\ \bar{a} \\ a \end{array} \quad \begin{array}{l} b \\ 1 \\ 1 \end{array} \rightarrow f = \bar{b} + \bar{a}$$

Prefrence :-  $2 < 4 < 6 < 8$ .

\*  $f = \sum_{SOP} (0, 5, 4, 7, 3)$

$\pi \rightarrow POS$

These values are positions.

$a'bc$	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$
00	0			
01	1			
11		1		
10			1	

a	b	c		1
0	0	0		1
0	0	1		1
0	1	0		1
0	1	1		1
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		1

$a'bc$	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$	$\bar{b}\bar{c}$
00	0				
01	1				
11	1	1	1	1	1
10	1	1	1	1	1

↳ This one is wrong because of 1 pair

$a'bc$	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$	$\bar{b}\bar{c}$
00	0				
01	1				
11	0	1	1	1	1
10	0	1	1	1	1

$$f = \bar{a}b + bc + \bar{b}\bar{c}$$

This represents SOP, if  $\pi$  is present, it represents POS.

Q.  $f = \sum_{SOP} (0, 2, 3, 4, 6)$

$a'bc$	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$
00	1			
01		1		
11			1	
10			1	

$$f = \bar{c} + \bar{a}b$$

a	b	c		1
0	0	0		1
0	0	1		1
0	1	0		1
0	1	1		1
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		1

Q.

$a'bc$	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$
00	1			
01		1		
11			1	
10			1	

$$f = \bar{a} + c$$

Q.

$a'bc$	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$
00	1			
01		1		
11			1	
10			1	

Sol<sup>n</sup>: -  $f = \bar{a} + b + c$

Q.

$a \backslash b$	$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	0   1   0   1   0	0   0   0   1   0	0   0   1   1   1	0   1   1   0   1
$a$	1   0   1   0   1	1   1   1   0   1	1   1   0   1   1	1   0   0   1   1



Sol<sup>n</sup>: -  $f = ab + \bar{b}\bar{c} + a\bar{c} + \bar{a}bc$

Q.

$a \backslash b$	$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	0   1   1   0   1	0   0   0   1   0	0   0   1   1   1	0   1   1   0   1
$a$	1   0   1   1   0	1   1   1   0   1	1   1   0   1   1	1   0   0   1   1

Sol<sup>n</sup>: -  $f = \bar{b} + \bar{c}$

# NOR

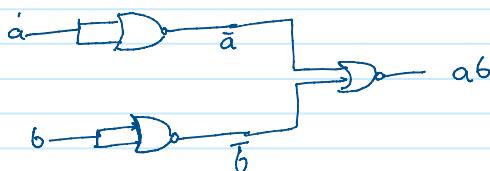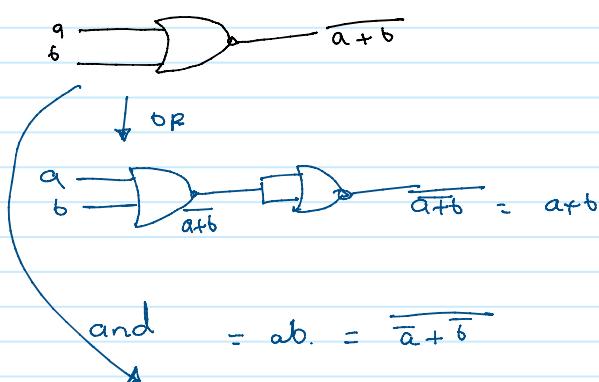


\*

$ab \backslash cd$	$\bar{c}\bar{d}$	$\bar{c}d$	$cd$	$c\bar{d}$
$\bar{a}\bar{b}$	00   0   1   3   2	00   0   0   1   0	00   0   1   1   1	00   1   0   0   1
$\bar{a}b$	01   4   5   7   6	01   0   0   0   0	01   0   1   0   1	01   1   0   1   0
$a\bar{b}$	11   12   13   15   14	11   0   0   0   0	11   0   1   0   1	11   1   0   1   0
$ab$	10   8   9   11   10	10   0   0   0   0	10   0   1   0   1	10   1   0   1   0

Q.  $f = \sum (0, 1, 4, 9, 10, 12)$


$\bar{c}\bar{d}$      $\bar{c}d$      $cd$      $c\bar{d}$

$\bar{a}\bar{b}$

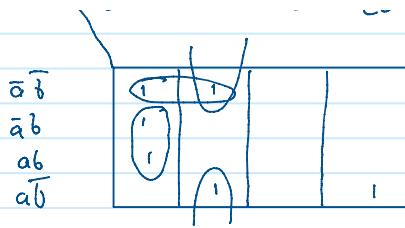

$$f = \bar{a}\bar{b}\bar{c} + b\bar{c}\bar{d} + \bar{b}\bar{c}\bar{d} + a\bar{b}cd$$


\*

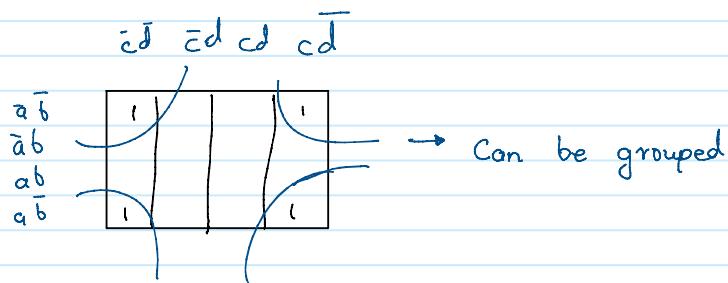

$$f = \bar{b}d$$

Q.

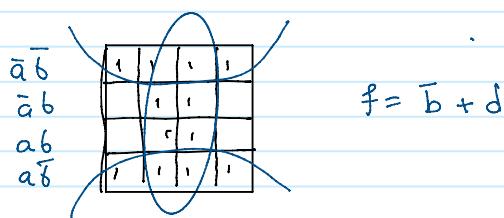
$$\bar{c}\bar{d} \quad \bar{c}d \quad c\bar{d} \quad cd$$



$$f = \bar{b} + d$$


Q.
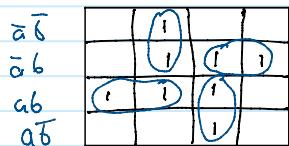
$$\bar{c}\bar{d} \quad \bar{c}d \quad cd \quad c\bar{d}$$




$$f = \bar{a}\bar{c}d + \bar{a}bc + acd + ab\bar{c}.$$

Q.

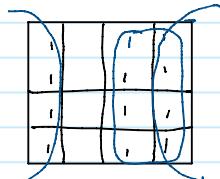

Q.

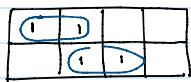

Q.

1	1	
1	1	

# Don't Care :-

a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	x → i don't care
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Q.

$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	1	1	x
a	1	1	1

Let,  $x = 0$

$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	1	0	0
a	1	1	1

$$f = \bar{a}\bar{c} + \bar{b}c$$

Let,  $x = 1$

$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	1	1	1
a	1	1	1

$$f = \bar{a} + \bar{b}c$$

1	1	1	1
1	1	x	

Soln:- Let,  $x = 1$

$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	1	1	1
a	1	1	1

$$f = \bar{a} + b$$

Let,  $x = 0$

$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	1	1	0
a	1	1	0

$$f = \bar{a} + bc$$

Q.

$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	1	1	1
a	1	1	1

Q.

$\bar{b}\bar{c}$	$\bar{b}c$	$bc$	$b\bar{c}$
$\bar{a}$	1	1	1
a	1	1	1

Q.

	$\bar{b}$	$\bar{c}$	$b$	$c$	
$\bar{a}$	1	1	1	1	X
a	1	1	1	1	

$$f = \bar{a}$$


Q.

	$\bar{b}$	$\bar{c}$	$b$	$c$	
$\bar{a}$	1	1	1	1	X
a	1	1	1	1	X


$$f = \bar{a} \bar{c}$$

# Combinational Circuit :-

→ Half-Adder :-

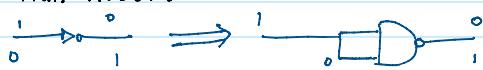

# NOR

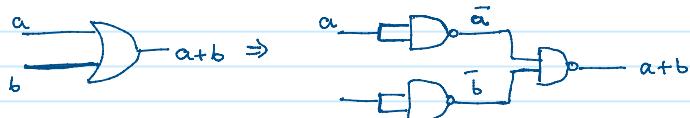

Q.



# XOR Gate [7486]  
OR Gate [7432]  
NOR Gate [ ]



XOR Gate

a	b	f
0	0	0
0	1	1
1	0	1
1	1	0

$$f = \underbrace{\bar{a} \cdot b + a \bar{b}}_{= a \oplus b} \rightarrow SOP$$


0	1	1
1	0	1
1	1	0

$$= a \oplus b$$

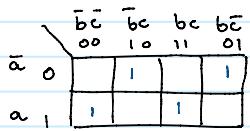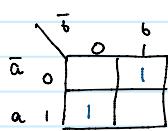


XOR Gate

$$f = a \oplus b \oplus c.$$

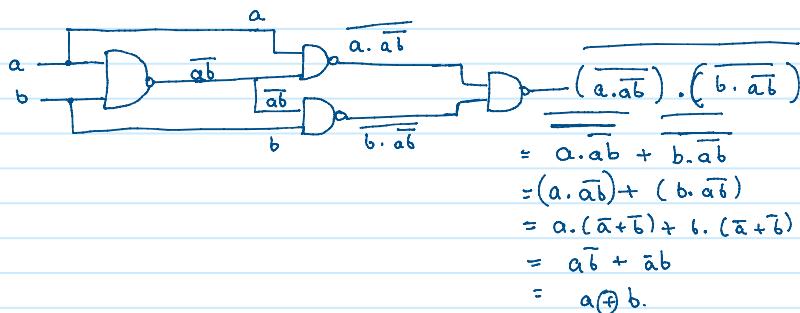

# XNOR Gate

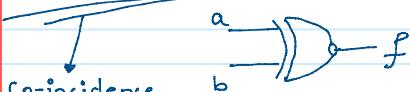

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

$$f = \bar{a}\bar{b} + ab$$

$$= a \odot b$$

$$\overline{f_{XOR}} = f_{XNOR}$$

$$\boxed{\overline{a \oplus b} = a \odot b}$$

$$\overline{\bar{a}\bar{b} + ab} = a \oplus b$$

$$\overline{\bar{a}b + \bar{a}\bar{b}} = a \odot b$$

# Half-Adder :-


Only applicable for 2-bit operations.

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = \bar{a}b + a\bar{b} = a \oplus b$$

$$\text{Carry} = ab$$



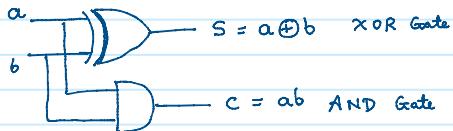

## # Full-Adder

Applicable for 3 bit.

	a	b	c	sum	carry
①	0	0	0	0	0
②	0	0	1	1	0
③	0	1	0	1	0
④	0	1	1	0	1
⑤	1	0	0	1	0
⑥	1	0	1	0	1
⑦	1	1	0	0	1
	1	1	1	1	1

$$\text{Sum} = \sum (1, 2, 4, 7)$$

Full Adder

$$\text{Sum} = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}c + abc$$

$\bar{a}$	1	1	1
a	1	1	1

$$f = a \oplus b \oplus c$$

$$\text{Carry} = \sum (3, 5, 6, 7)$$


$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$
$\bar{a}$	1	1	1
a	1	1	1

$$\text{Carry} = ab + bc + ca$$


$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	$bc$
$\bar{a}$	1	1	1
a	1	1	1

$$\begin{aligned} * \text{Carry} &= \bar{a}\bar{b}c + \bar{a}\bar{b}c + ab \\ &= c(\bar{a}b + a\bar{b}) + ab \\ &= c(a \oplus b) + ab. \end{aligned}$$

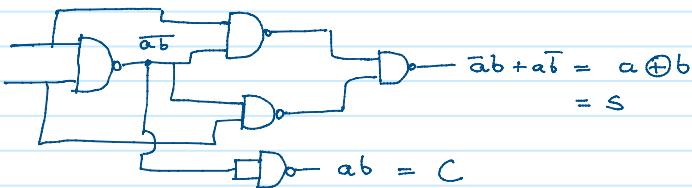
- Q. For developing a Half-Adder, how many NAND Gates are required.



# Full-Adder Circuit diagram :-

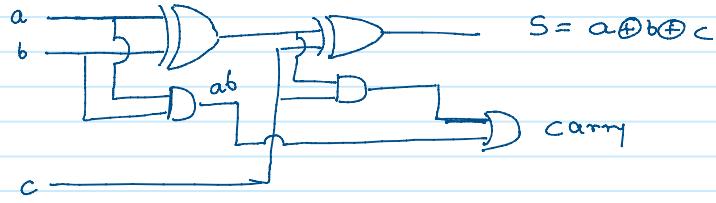

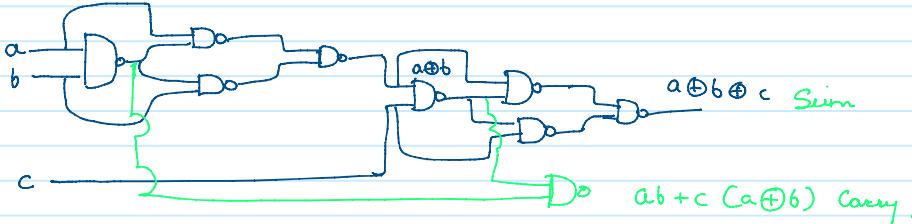
# Design a Full Adder using NAND Gate only.




# Half-Subtractor

a	b	[Difference]	[Borrow]
0	0	0	0
0	1	0	1
1	0	1	0
1	1	0	0

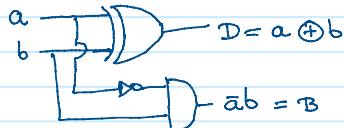
$D = \bar{a}b + a\bar{b} = a \oplus b$   
 $B = \bar{a}b$


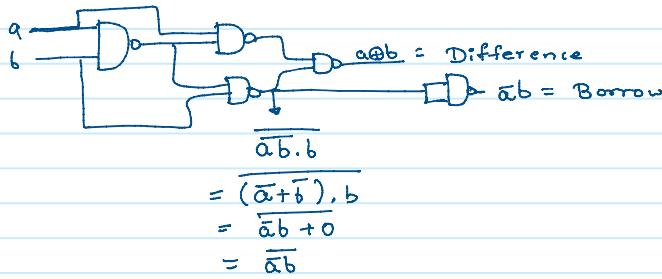
# Design a half-subtractor using NAND Gate only.


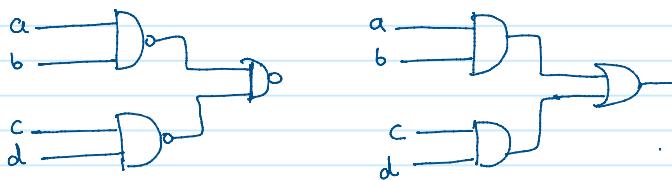
$$f = ab + cd \rightarrow [\text{AND-OR}]$$




NAND-NAND

AND OR



\*  $f = (a+b)(c+d) \rightarrow \text{OR AND Logic or}$   
 $\text{NOR NOR logic}$

# Convert this to NAND Gate.

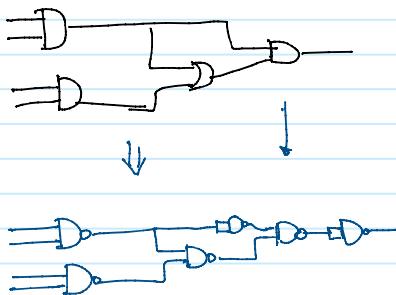


\*  $A \oplus A = 0$ ,  $A \odot A = 1$   
 $A \oplus \bar{A} = 1$ ,  $A \odot \bar{A} = 0$   
 $A \oplus 0 = A$ ,  $A \odot 0 = \bar{A}$   
 $A \oplus 1 = \bar{A}$ ,  $A \odot 1 = A$

Convert these to NAND Gate.

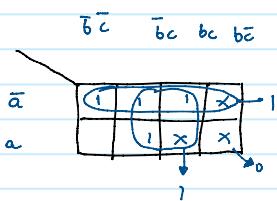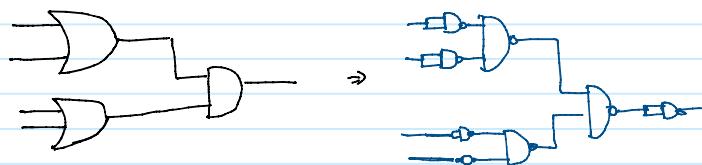


Thoda galat thi ise parallel bulana.

# Parallel Binary Adder:-

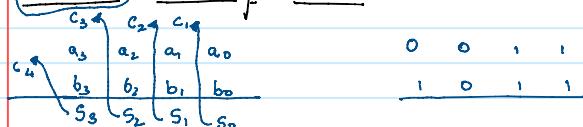

$$\begin{array}{r} 0 & 0 & 1 & 1 \\ 1 & 0 & 1 & 1 \end{array}$$

[Disadvantage  
→ Time delay]

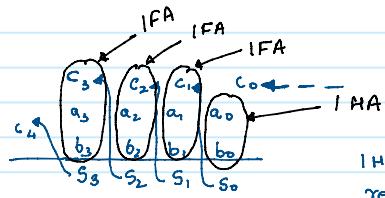

$$1 \text{ FA} + 3 \text{ FA}$$

$$1 \text{ HA} + 3 \text{ OR gate}$$

required

$$\begin{aligned} &1 \text{ HA} + 2 \text{ HA} + 2 \text{ HA} + 2 \text{ HA} + 3 \text{ OR} \\ &= 7 \text{ Half adder} + 3 \text{ OR gate} \end{aligned}$$

→ For 2-n bit, how many Full Adder required?

→ n - full adder

For addition

$$= (n-1) FA + 1 HA.$$

$$= (n-1)(2HA + 1OR) + 1HA$$

$$= (n-1)(2HA) + (n-1)(OR) + 1HA$$

For  $n=10$ ,

$$= 18 HA + 9OR + 1HA$$

$$= 19HA + 9OR$$


## # Surprise Test :-

Q.1  $f = \sum (0, 1, 2, 3, 4, 5) + d(6)$

Q.2.  $f = \prod (0, 1, 2)$

Q.3.  $f = ABC + \bar{A}BC + BC + AC$  [form the standard SOP]

Q.4.  $f =$

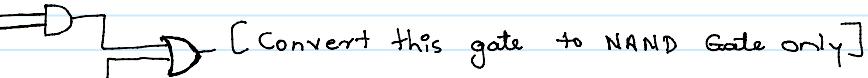

[Convert this gate to NAND Gate only]

Soln:-

Q1. 
$$\Rightarrow f = \bar{a} + \bar{b}$$
 [Don't care ki yaha koi jarurat nahi]

Q2. 
$$f = ab$$

$\bar{a} \quad \bar{b}$   
 $a \quad b$   
SOP form  
 $f = ab$

Q3.  $f = ABC + \bar{A}BC + BC + AC$

$$= BC(A + \bar{A}) + BC + AC$$

$$= BC + BC + AC$$


BC

$$= BC + AC$$

$$= C(A+B)$$

9861480775  
↳ Prof. P. Biswas  
Sir ka number

Q.4.

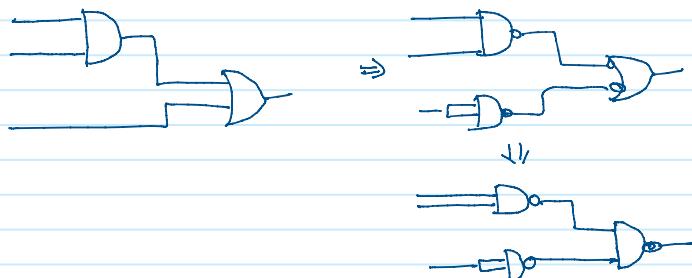



15-09-2023

Q.  $\begin{array}{cccc} c_3 & c_2 & c_1 \\ a_3 & a_2 & a_1 & a_0 \\ \hline b_3 & b_2 & b_1 & b_0 \\ \hline s_3 & s_2 & s_1 & s_0 \end{array}$

For producing sum, it takes 6 ns  
For producing carry, it takes 3 ns.

For  $c_1 \rightarrow$  we need 3 ns  
+ For  $c_2 \rightarrow$  we need 3 ns  
+ For  $c_3 \rightarrow$  we need 3 ns  
 $\frac{9 \text{ ns}}{= 3 \times (3 \text{ ns})}$

For adding  $a_3$  and  $b_3$   
we will need 6 ns

Total time required =  $9 + 6 = 15 \text{ ns}$ .

In general, if 'n' is number of bit,  
we can say

$$(n-1) \times [\text{time taken by a carry}] + [\text{Time taken by sum}]$$

Q. For  $\begin{array}{c} c_3 \\ a_3 \\ b_3 \\ \hline s_3 \end{array} \quad \begin{array}{c} c_2 \\ a_2 \\ b_2 \\ \hline s_2 \end{array} \quad \begin{array}{c} c_1 \\ a_1 \\ b_1 \\ \hline s_1 \end{array} \quad \begin{array}{c} c_0 \\ a_0 \\ b_0 \\ \hline s_0 \end{array}$

a) How many full adder is required?  
 $\Rightarrow 4$


b) How many HA and Full adder, required  
 $\Rightarrow 3$  Full Adder and 1 Half adder

Q. For 13 bit group addition,  
a) How many full adder is required - 13 FA  
b) How many Full adder and Half adder is required  
 $\hookrightarrow 12 \text{ FA and } 1 \text{ HA}$


c) How many Half adder are required

24 HA + 10 Gate

# For subtraction :-

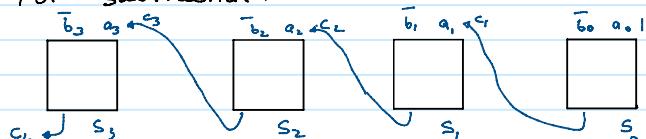

Input

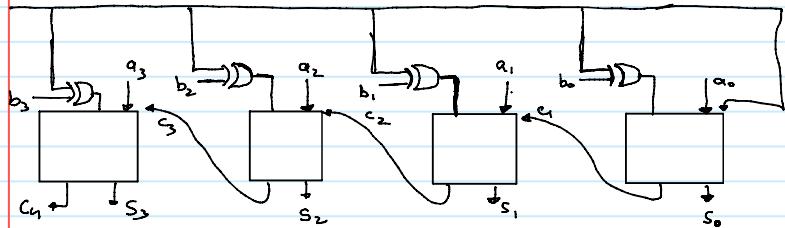

If input is 0, Add  
If input is 1, Subtract

$$f = ny + nw + yw \\ = ny + yw \quad [\text{consensus}]$$

# Carry Look Ahead Addition.

For a 3-bit addition

a	b	$c_i$	s	$c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1 →
1	0	0	1	0
1	0	1	0	1 →
1	1	0	0	1 →
1	1	1	1	1 →

$$C_{i+1} = ab + (a \oplus b) \cdot c_i$$

$\underbrace{ab}_{\text{Carry Generator } [G]}$        $\underbrace{(a \oplus b) \cdot c_i}_{\text{Carry Propagator } [P]}$

$$\Rightarrow C_{i+1} = G_i + P_i c_i$$

$$\Rightarrow C_1 = G_0 + P_0 c_0$$

$$C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 (G_0 + P_0 c_0)$$

$$= G_1 + P_1 G_0 + P_1 P_0 c_0$$

$$\begin{array}{ccccccc} & & & & c_1 & & \\ & a_3 & a_2 & a_1 & a_0 & & \\ & b_3 & b_2 & b_1 & b_0 & & \\ \hline & & & & c_1 & & \end{array}$$

$G = ab$   
 $P = a \oplus b$

$$C_3 = G_2 + P_2 C_2$$


$$= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 c_0)$$

$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$C_4 = G_3 + P_3 C_3$$


$$= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0)$$

22-09-2023

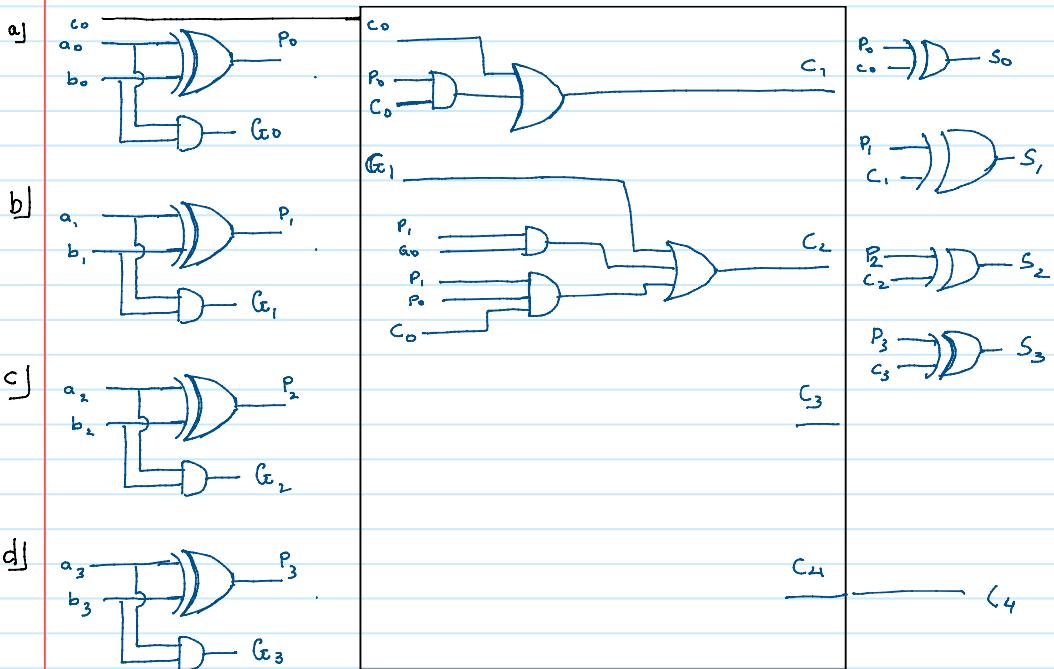


Time will remain same as all the inputs are given at once

### # Decoder :-

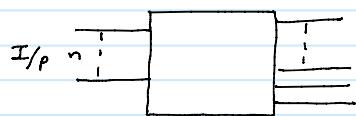


$2^n$  O/P

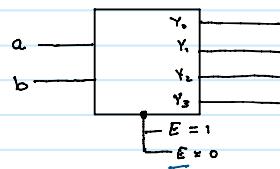



a	b	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

} Active High Logic

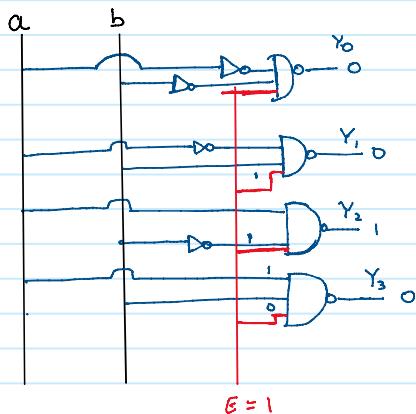

### # Full Adder :-

Full Adder

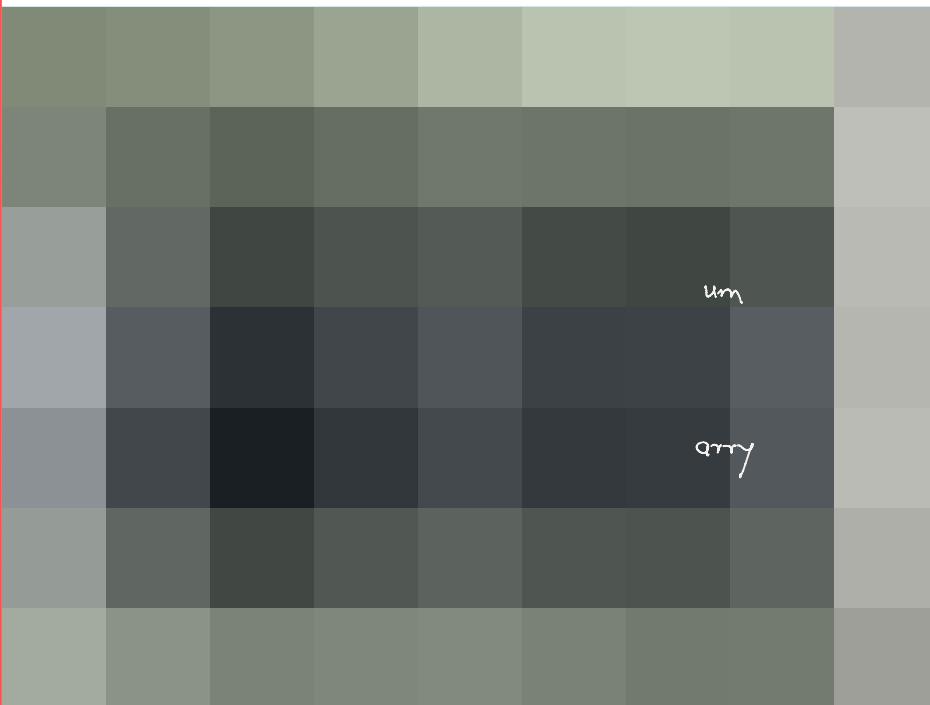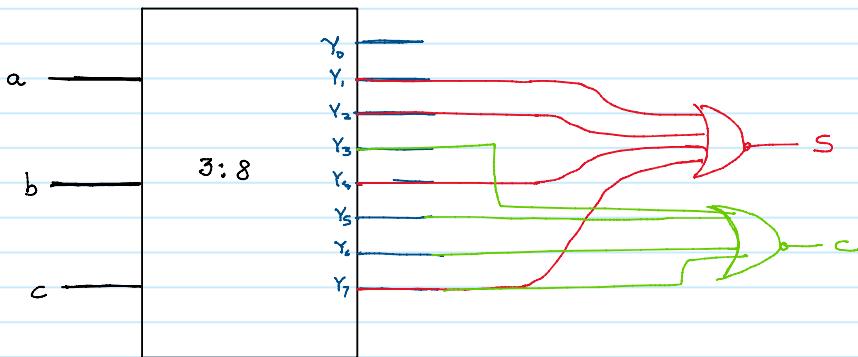

$$S = \sum (1, 2, 4, 7) \rightarrow \text{SOP of sum}$$


$$C = \sum (3, 5, 6, 7) \rightarrow \text{SOP of carry.}$$

# Designing this circuit using AND Gate:-



NAND ke aage NOT Gate laga do!


If,

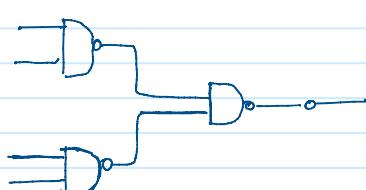

this gives you SOP,



then,

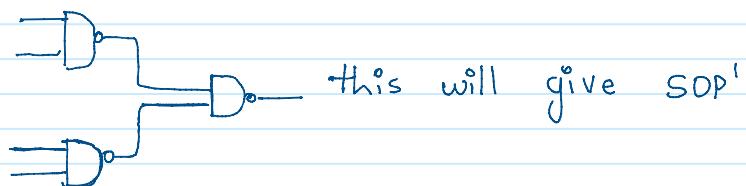



NAND AND - POS

NAND NAND - SOP


AND NOR - POS

AND OR - SOP.


Q Design 3:8 decoder using 2:4 decoder:-

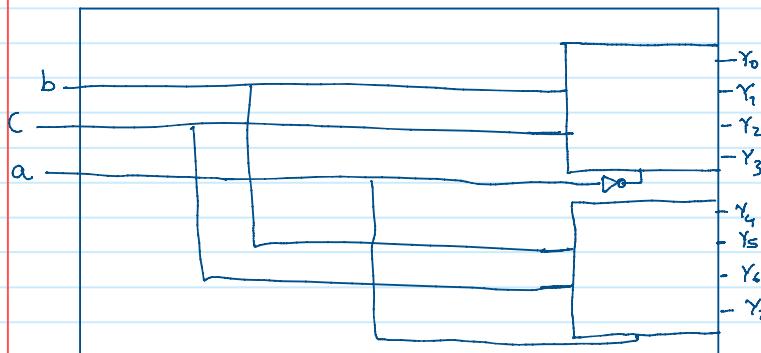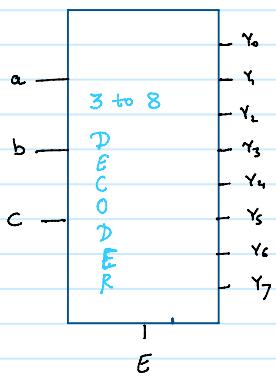

Q. Design 4:16 decoder using 2:4 decoder

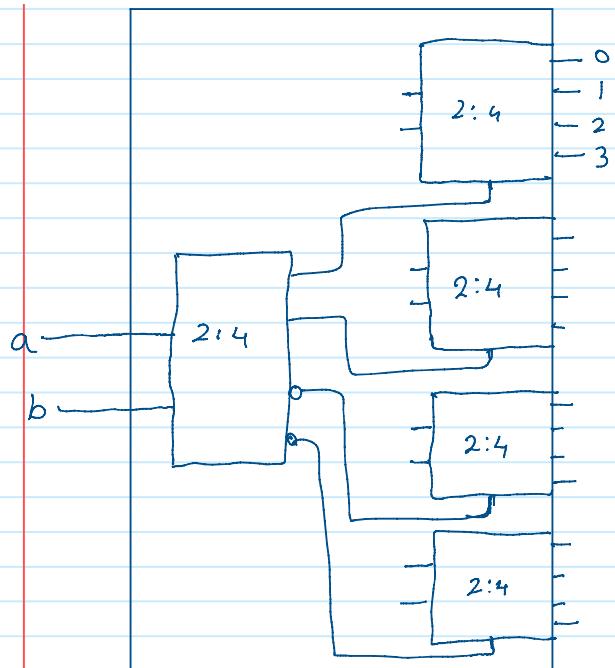

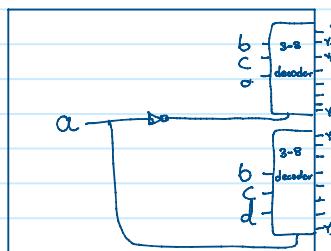Q. Design a 4:16 decoder using 3:8 decoder






A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

# Binary to Gray Code :-

→ 3-bit binary to gray code logic

a	b	c	g <sub>1</sub>	g <sub>2</sub>	g <sub>3</sub>
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

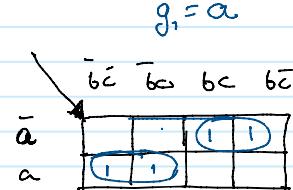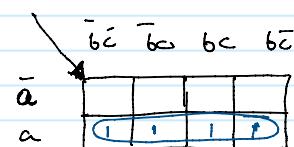

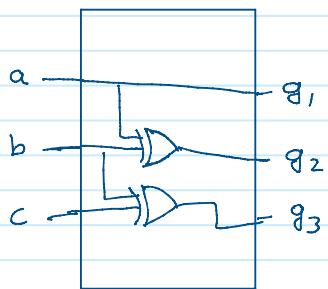

$$g_2 = \bar{a} + \bar{b}$$


$$= a \oplus b$$

$$g_3 = b \oplus c$$

# BCD to 7 segment display :-

B C D	A B C D	a b c d e f g	$\frac{a}{g}$	$\frac{b}{g}$	$\frac{c}{g}$	$\frac{d}{g}$
0 0 0 0	0 0 0 0	1 1 1 1 1 0				→ 0
0 0 0 1	0 0 0 1	0 1 1 0 0 0 0				
0 0 1 0	0 0 1 0	1 1 0 1 1 0 1				→ 2
0 0 1 1	0 0 1 1	1 1 1 1 0 0 1				→ 3
0 1 0 0	0 1 0 0	0 1 1 0 0 1 1				
0 1 0 1	0 1 0 1	1 0 1 0 1 1 1				
0 1 1 0	0 1 1 0	1 0 1 1 1 1 1				→ 6
0 1 1 1	0 1 1 1	1 1 1 0 0 0 0				→ 7
1 0 0 0	1 0 0 0	1 1 1 1 1 1 1				→ 8
1 0 0 1	1 0 0 1	1 1 1 1 0 1 1				→ 9

for d,

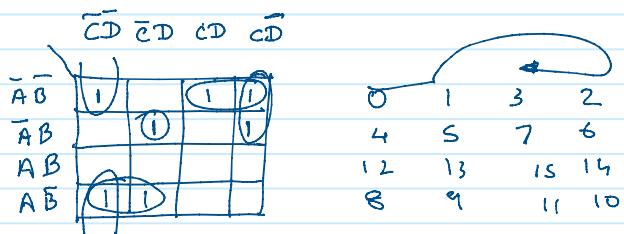


$$f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}C\bar{D} + A\bar{B}\bar{C} + \bar{A}B\bar{C}\bar{D}$$
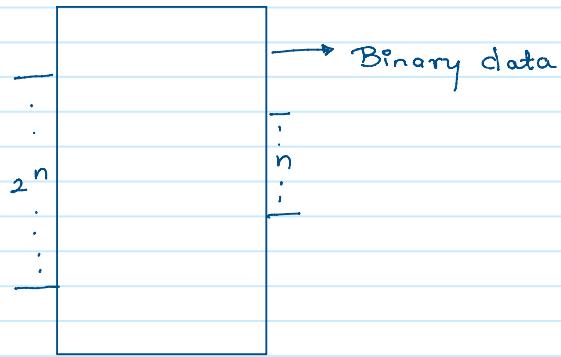
# Encoder :-

↳ Saral bhosha mai ye bhi decoder ki tarah ek convertor hai.

- $2^n$  input → kisi bhi form me input ho sakte hai [Octal, Hexadecimal, etc.]
- $n$  output → output binary hi hogा.



→ 4:2 Encoder :-

$A_0$	$A_1$	$A_2$	$A_3$	$Y_0$	$Y_1$	$V$
X	X	X	X	X	X	O
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1


Valid pin  
If 0, input is nothing.

If 1, check output


Priority Encoder :-  
highest priority will be considered for output,

Lower priority bit will not be considered


$Y_0$ ,

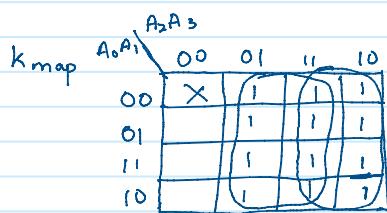

$$Y_0 = A_2 + A_3$$

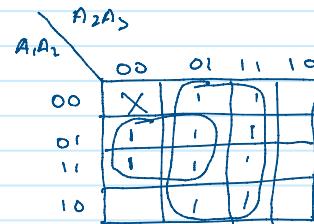

$$Y_1 = A_3 + A_1 \bar{A}_2$$

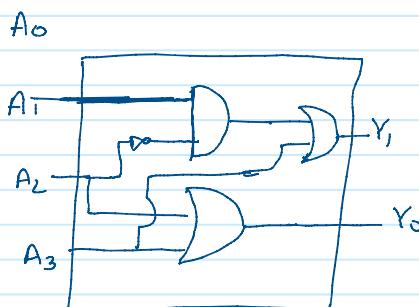





5-October-23

$$\begin{array}{r}
 \text{Q1.a)} \quad -14 \\
 -\underline{-6} \quad \rightarrow \quad -14 \\
 \end{array}
 \quad
 \begin{array}{r}
 \rightarrow +6 \\
 +\underline{6} \quad \rightarrow \quad +6 \\
 \end{array}
 \quad
 \begin{array}{r}
 \rightarrow +6 \\
 -\underline{-14} \quad \rightarrow \quad -14 \\
 \end{array}
 \quad
 \begin{array}{r}
 \rightarrow 0110 \\
 +\underline{0010} \\
 \hline
 1000
 \end{array}$$

14 → 1110  
 → 2's complement  
 0010

↴ number is negative.  
 -8 → Answer.

$$\begin{aligned}
 \text{Q1.b)} \quad & PQ' + PR + QR' = P + QR' \\
 & = PQ'(R+R') + PR(Q+Q') + QR'(P+P')
 \end{aligned}$$


$$= \underline{PQ'R} + \underline{PQ'R'} + PRQ + \underline{PRQ'} + PQR' + P'QR'$$

	$\bar{Q}\bar{R}$	$Q\bar{R}$	$QR$	$Q\bar{R}$
$\bar{P}$	1	1	1	1
$P$	1	0	1	0


$$F = P + QR$$

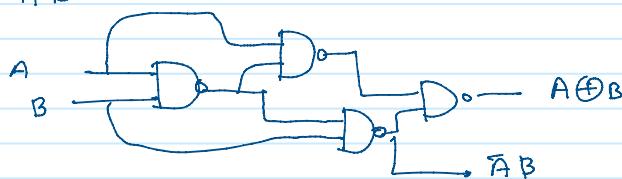Q1.c) Half subtractor using 2 NAND Gate

$$\begin{aligned}
 D &= A \oplus B \\
 B &= \bar{A}B
 \end{aligned}$$



Q1.d

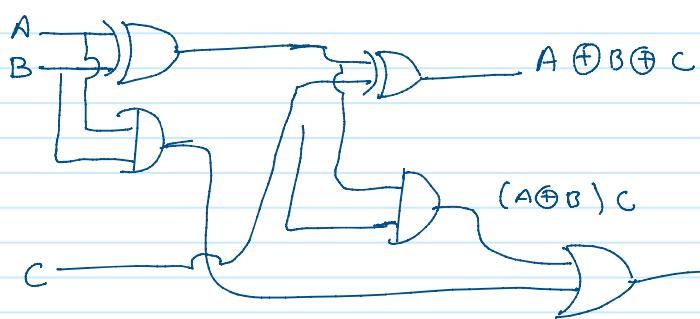

Q1.e.

$$\begin{array}{r} 858 - 749 \\ - \\ \hline 1000 & 0101 & 1000 \\ -0111 & 0100 & 1001 \\ \hline 0001 & 0000 & 1111 \\ -0110 \\ \hline 0001 & 0000 & 1001 \\ \hline \end{array}$$

1 0 9


$$\begin{array}{r} + 0001\ 1001 \\ 0001\ 0100 \\ \hline 0010\ 1101 \\ + 0110 \\ \hline 0011\ 0011 \\ \hline \end{array}$$

$+ 19$   
 $\underline{\quad 14}$   
 $\underline{\quad 33}$

Q2.  $\Sigma(0, 1, 2, 9, 11, 15), d(2, 4)$ 

	$\bar{B}\bar{D}$	$\bar{B}D$	$BD$	$B\bar{D}$
$\bar{A}\bar{B}$	x	1	1	x
$\bar{A}B$	x	1	1	1
$A\bar{B}$	1	1	1	x
$AB$	1	1	1	1

$$f = B\bar{D} + \bar{A}\bar{C}D + BC$$

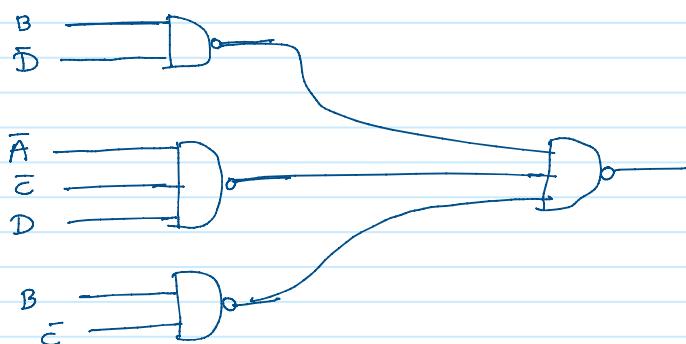


$$\Sigma(0, 1, 2, 9, 11, 15) \quad d(8, 10, 14) \\ \Pi(3, 4, 5, 6, 7, 8, 10, 12, 13, 14, 16)$$

$$\sum(0, 1, 2, 9, 11, 15) \quad d(8, 10, 14) \\ \Pi(3, 4, 5, 6, 7, 8, 10, 12, 13, 14, 16)$$


$\frac{y^2}{(y+z)(y+\bar{z})(\bar{y}+z)} \quad d($

$w+x$	$00$	$01$	$10$
$w+\bar{x}$	$01$	$00$	$00$
$\bar{w}+x$	$11$	$00$	$x$
$\bar{w}+\bar{x}$	$10$	$x$	$x$
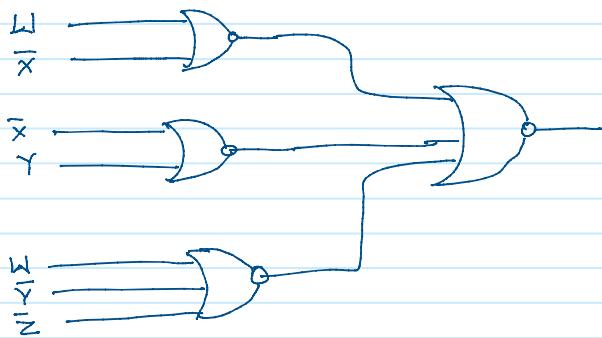
$$f = (w+x) \cdot (\bar{x}+y) \cdot (\bar{w}+\bar{y}+z)$$



3	$m$	$y$	$z$	$A$	$B$	$C$
	0	0	0	0	0	1
	0	0	1	0	1	0
	0	1	0	0	1	1
	0	1	1	3	1	0
	1	0	0	0	1	1
	1	0	1	5	0	0
	1	1	0	6	0	1
	1	1	1	7	1	0

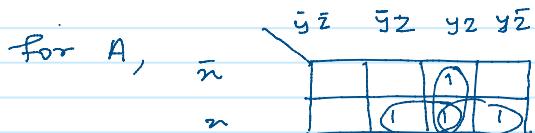

$$f = nz + yz + ny = A \\ = B \\ = C$$

4	$A_3$	$A_2$	$A_1$	$A_0$	$B_3$	$B_2$	$B_1$	$B_0$
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	1	1	1
0	0	1	0	0	1	1	1	0
0	0	1	1	0	1	1	0	1
0	1	0	0	0	1	1	0	0
0	1	0	1	1	1	0	1	1

0	1	1
0	1	0
0	1	0
0	1	0
0	1	1
0	1	1
1	0	0
1	0	0
1	0	0
1	0	1
1	0	1
1	0	1
1	1	0
1	1	0
1	1	0
1	1	0
1	1	1
1	1	1

Q4

