

Bipolar Junction Transistor

①

- Developed by William Shockley
- which can amplify electronic signal.

Bipolar


b/c current conduction is responsible by two types of charge carriers (Both Electron & Hole)

- The Device has three Terminal

- Emitter (heavily Doped)
- Base (very lightly Doped)
- Collector (lightly Doped)
Moderately Doped


- It has two Junctions

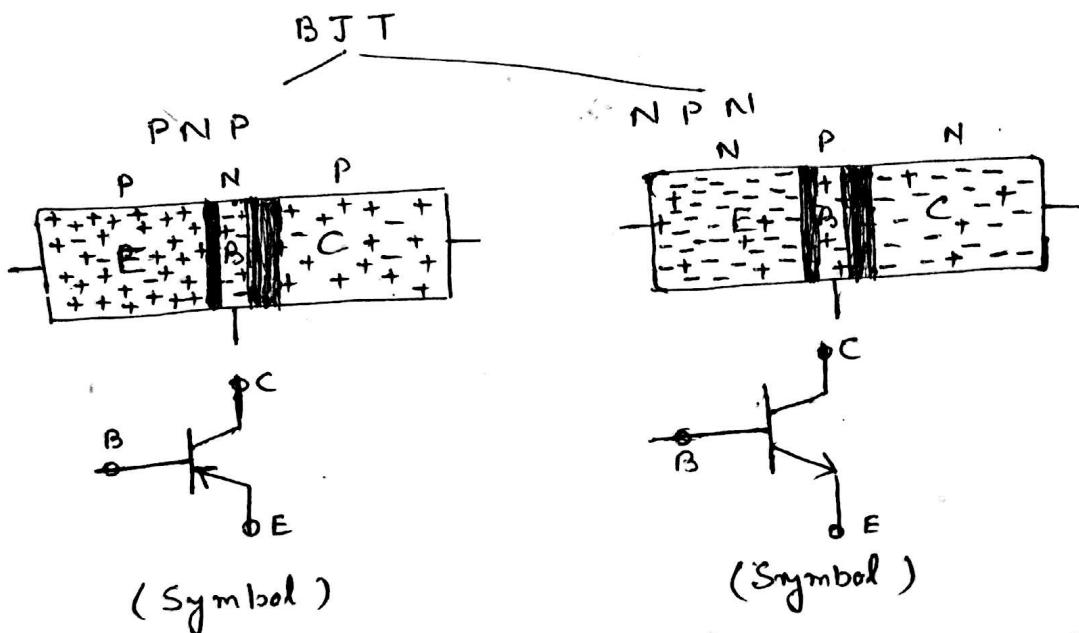- Base Emitter Junction
- Collector Base Junction



- The arrowhead at emitter shows the current direction of the device.

Unbiased Transistor

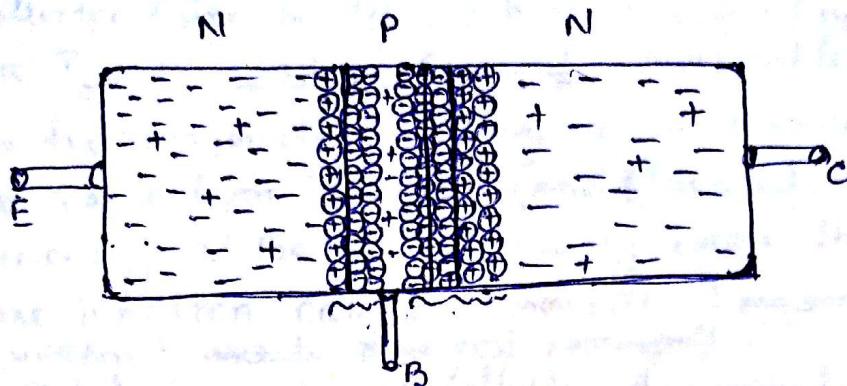


- The depletion region penetrates more deeply into the lightly doped side.
- Collector is less doped than emitter so the depletion width is higher at collector base junction than emitter base junction.

Transistor Operation

	<u>Base Emitter Junction</u>	<u>Collector Base Junction</u>
Active -	Forward Biased	Reverse Biased
Cutoff -	Reverse Biased	Reverse Biased
Saturation -	Forward Biased	Forward Biased

Active Operation

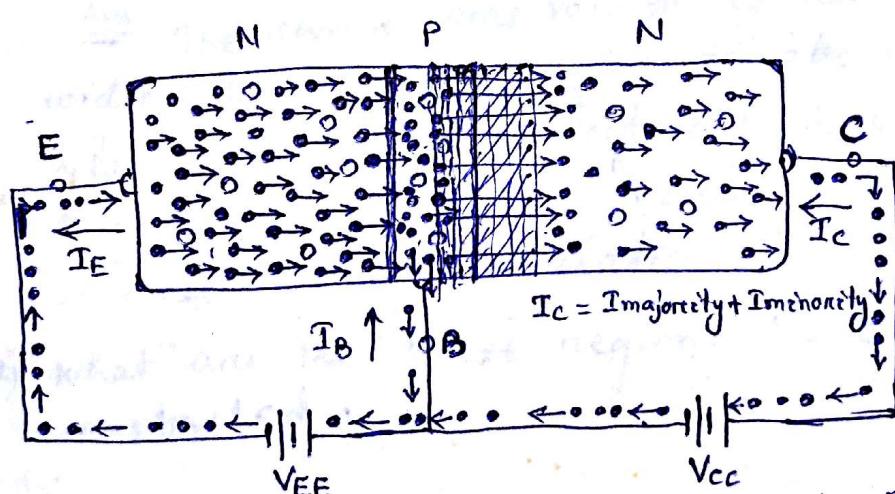• Base Emitter is Forward Biased
• Collector Base is Reverse Biased.



- The majority carriers flow from emitter to base through the Base Emitter junction (Forward Biased).
- Some of the majority carriers flow through the Base Collector junction (Reverse Biased) as minority carriers at Base.
- The Collector Base junction is increased due to Reverse Bias and there will be no flow of majority carriers.

- The minority carriers of the Base will flow the collector Base junction, which causes I_{minority} or I_{C0} or Leakage Current. (Undesirable)
- And the majority carriers from emitter who are came from emitter (and treated as minority at Base) can easily cross the collector base junction caused current I_{majority} (The desired current) ~~due to injected carrier~~.
- So Total current at collector terminal is

$$I_C = I_{\text{majority}} + I_{\text{minority}}$$

- Finally the fundamental current relation is

$$\boxed{I_E = I_B + I_C}$$

(Q) In a transistor emitter current is 1.02 times larger from collector current. If $I_E = 12 \text{ mA}$ then find Base current.

(Q) Draw the schematic of an NPN transistor indicating various current components and explain how each one of them arises.

(Q) What do you mean by Early Effect or Base Width Modulation.



Ans The reverse bias voltage increases, the width of depletion region also increases. Which reduces the electrical Base width, this effect is called "Early Effect" or "Base Width Modulation".

(Q) What are the three regions the BJT constructed.

Transistor Configuration


Common Base (CB) Common Emitter (CE) Common Collector (CC)

Common Base →

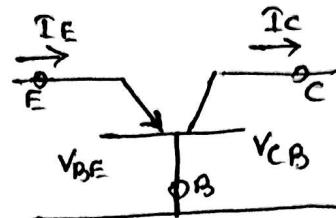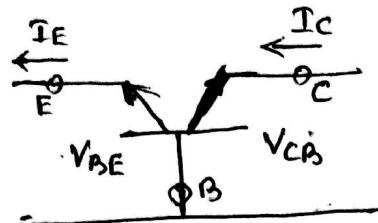



The Current Amplification factor

$$\alpha = \frac{I_C}{I_E}$$


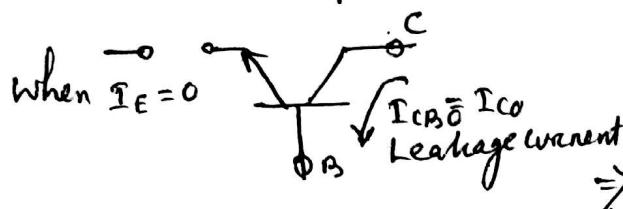


$$\Rightarrow \alpha = \frac{I_C - I_{CBO}}{I_E}$$

$$I_C = \alpha I_E + I_{CBO}$$

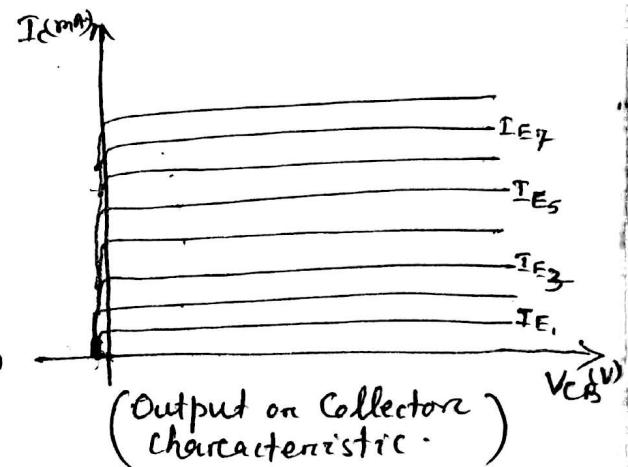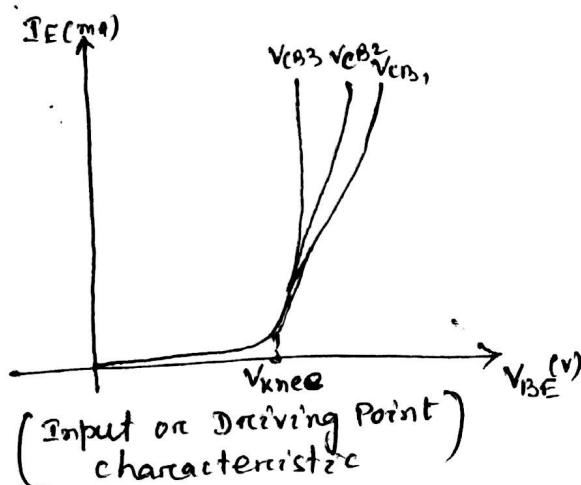


Common Emitter →

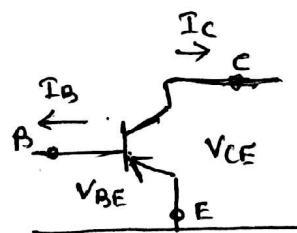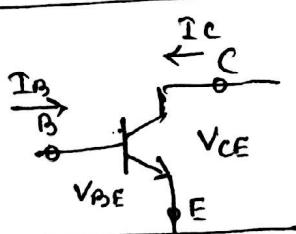


The Current Amplification factor


$$\beta = \frac{I_C}{I_B}$$

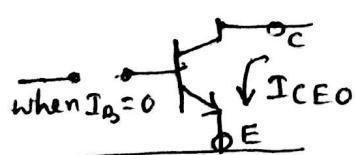
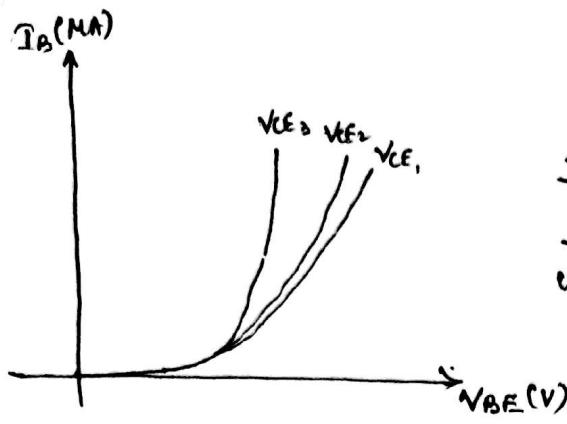
$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \quad \text{with } I_B = 0 \text{ mA}$$





(Input or Base characteristic)

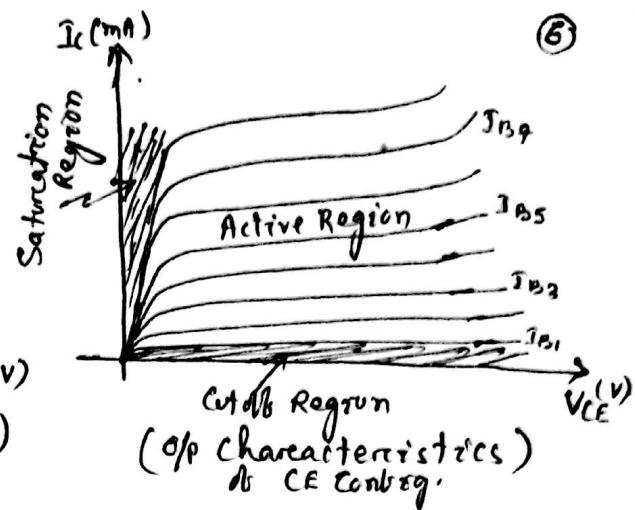


(O/p characteristics)
As CE Config.

Common Collector →

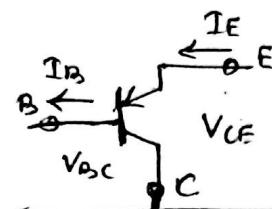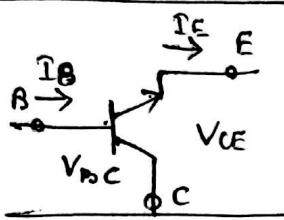


The current amplification factor

$$\beta = \frac{I_E}{I_B}$$

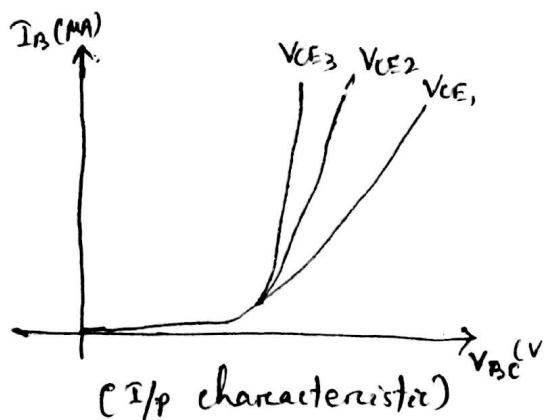

(I/p characteristic)

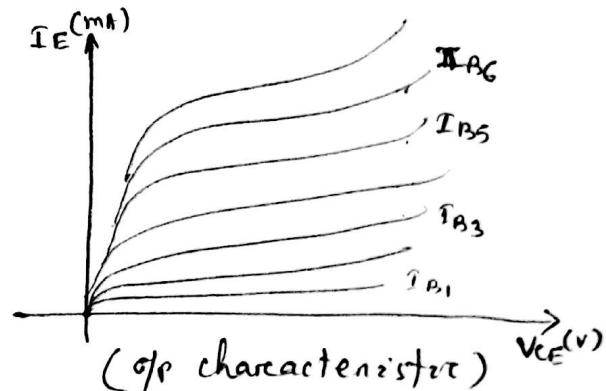

(O/p characteristic)

Current Relations

$$\text{From CB config } I_C = \alpha I_E + I_{CB0}$$

$$\Rightarrow I_C - I_{CB0} = \alpha I_E$$

$$\Rightarrow \frac{I_C}{\alpha} - \frac{I_{CB0}}{\alpha} = I_E = I_B + I_C$$

$$\Rightarrow I_C \left[\frac{1}{\alpha} - 1 \right] = I_B + \frac{I_{CB0}}{\alpha}$$

$$\Rightarrow I_C = \left(\frac{\alpha}{1-\alpha} \right) I_B + \left(\frac{1}{1-\alpha} \right) I_{CB0}$$

$$\Rightarrow I_C = \beta I_B + \left(\frac{1}{1-\alpha} \right) I_{CB0} \quad [\because \beta = \frac{\alpha}{1-\alpha}]$$

$$\Rightarrow I_C = \beta I_B + (1+\beta) I_{CB0} \quad [\because 1 + \frac{\alpha}{1-\alpha} = \frac{1}{1-\alpha}]$$

This term is Reverse Leakage Current

$$I_{CEO} = (1+\beta) I_{CB0}$$

$$(B) \text{ Prove } \alpha = \frac{\beta}{\beta + 1}$$

Ans We know $I_E = I_B + I_C$

$$\Rightarrow \frac{I_C}{\alpha} = \frac{I_C}{\beta} + I_C$$

$$\therefore \alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

$$\Rightarrow \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\Rightarrow \frac{1}{\alpha} = \frac{1+\beta}{\beta}$$

$$\Rightarrow \boxed{\alpha = \frac{\beta}{1+\beta}}$$

$$(a) \text{ Prove}_{(a)} \beta = \frac{\alpha}{1-\alpha}$$


$$(b) I_E = (1+\beta) I_B$$

$$(c) \frac{1}{1-\alpha} = \beta + 1$$

$$(d) I_C = \frac{\alpha}{1-\alpha} I_B + \frac{I_{CBO}}{1-\alpha}$$

Transistor Amplifying Action

in a CB configuration

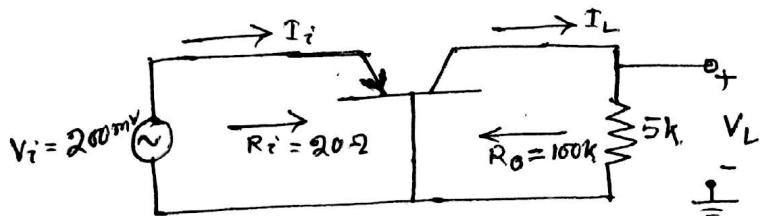

$$\text{Hence } I_i = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

As it is a CB config., assuming $\alpha = 1$ (by $I_C \approx I_E$)

$$I_L = I_i = 10 \text{ mA}$$

$$\text{So } V_L = I_L R \\ \approx (10 \text{ mA}) 5 \text{ k}\Omega = 50 \text{ V}$$

$$\text{So Voltage Gain} = A_v = \frac{V_L}{V_i} = \frac{50 \text{ V}}{200 \text{ mV}} = 250$$

So the basic amplifying is —

Low Resistance \Rightarrow High Resistance Amplifying
Transferring the Current →

✓ Transfer + Resistor = Transistor


(Q) For a transistor $\beta = 100$ and voltage drop across $R_C (2k\Omega)$ is 2 Volts . find the Base current for given ckt.

(8)



Ans

$$I_C = \frac{V_{RE}}{R_C} = \frac{2V}{2k\Omega} = 1mA$$
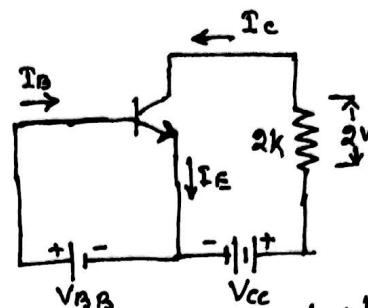
$$I_B = \frac{I_C}{\beta} = \frac{1mA}{100} = 10\mu A$$



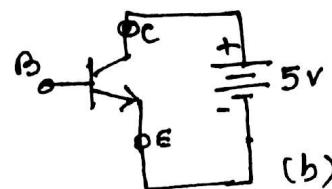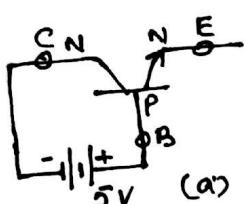(Q) An npn transistor has its emitter open and its collector current at room temperature is $0.2\mu A$ as shown in fig (a). For the same transistor if its base is kept open its collector current at room temperature is $20\mu A$ as shown in fig (b). Find α , I_E and I_B when collector current is $2mA$.



Ans In fig (a) The current $I_C = I_{CB0} = 0.2\mu A$
In fig (b) The current $I_{CEO} = 20\mu A$

$$I_{CEO} = \frac{I_{CB0}}{1-\alpha}$$

$$\Rightarrow 20\mu A = \frac{0.2\mu A}{1-\alpha} \Rightarrow \boxed{\alpha = 0.99}$$

$$\text{Hence } I_C = 2mA$$

$$\text{So } I_C = \alpha I_E + I_{CB0}$$

$$\Rightarrow 2mA = 0.99 I_E + 0.2mA$$

$$\Rightarrow I_E = \frac{2 * 10^{-3} - 0.2 * 10^{-6}}{0.99}$$

$$\Rightarrow \boxed{I_E = 2.02mA}$$

$$I_B = I_E - I_C$$

$$= 2.02mA - 2mA$$

$$\Rightarrow \boxed{I_B = 0.02mA}$$

(Q) Sketch the o/p characteristic of NPN Bipolar Junction Transistor in common emitter configuration . Indicate Active , Cutoff & Saturation Region .

Analysis or Design of BJT Amplifiers

⑨

DC Analysis

AC Analysis

DC Biasing


When a network is designed using BJT 1st it is desired to achieve a fixed level of dc-current & voltages at BJT.




To achieve a fixed level of dc current & voltage different networks with different dc supply provided to BJT known as Biasing.

Biased Networks


① Fixed Bias

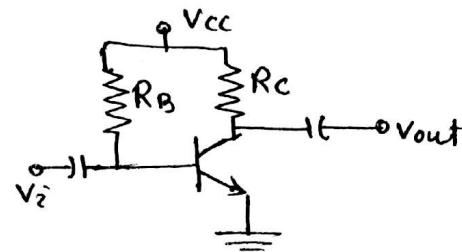

② Emitter Stabilized Bias

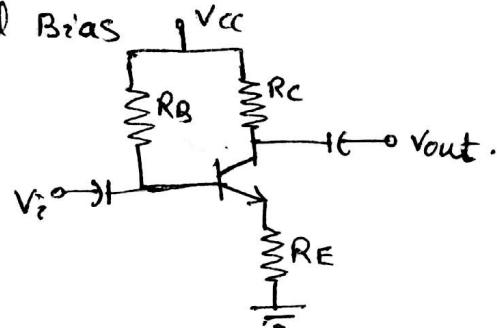

③ Voltage Divider Bias

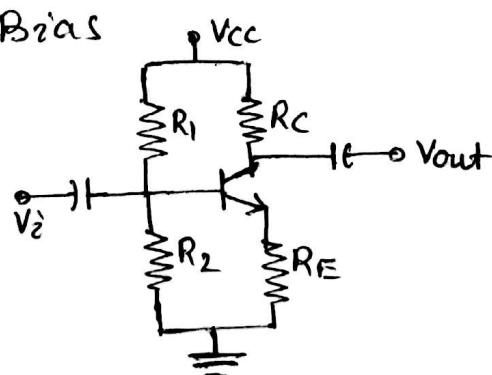


⑧

Operating Point or Bias Point

or Q-Point or Quiescent Point

- It is the intersection point of load line and O/P characteristic curve on O/P characteristic.
- Load line is a line between max current & maximum voltage of a given network. ($V_{CE\max}$ & $I_{C\max}$)
- The Q-point indicates the dc current (I_{CQ}) & dc voltage (V_{CEQ}) achieved by a particular network with a particular biased circuit.

As example
in a CE config

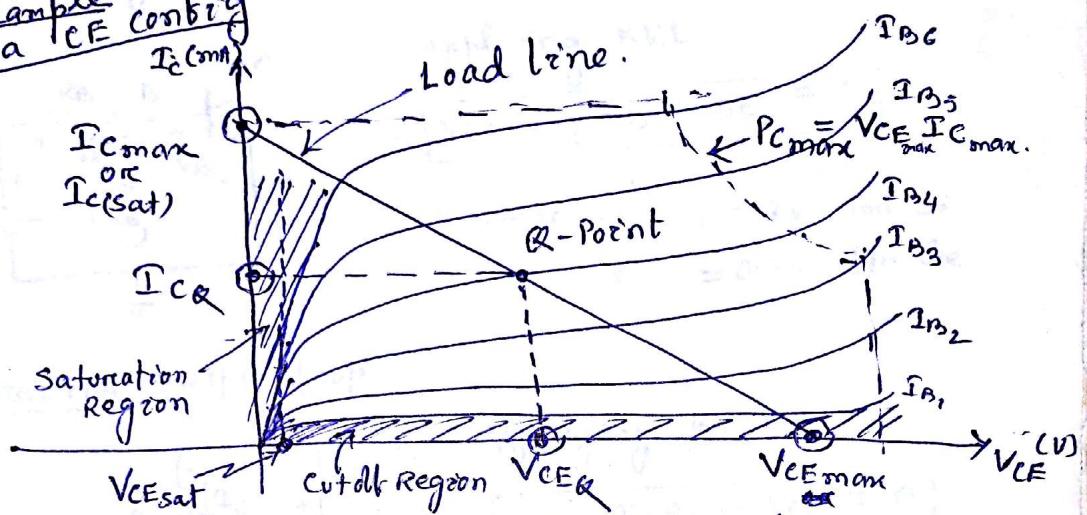

Let a CE configuration network gives

maximum o/p on collector current = $I_{C\max}$ or $I_{C(sat)}$

maximum o/p on Collector to Emitter Voltage = $V_{CE\max}$

& for the particular network the Base current is

$$I_B = I_{B4}$$

\therefore So the Q-Point will be as shown in figure.

The intersection Point = (V_{CEQ}, I_{CQ})
or Bias Point

Note

The operating point is changed if the biasing of the network is changed.

(11)

Fixed Biased Circuit Analysis


- When we go for dc analysis

the capacitor will be treated as open ckt.

- Analysis performed by considering two Loops


Base Emitter loop
or
Input Loop

Collector Emitter loop
or
Output Loop

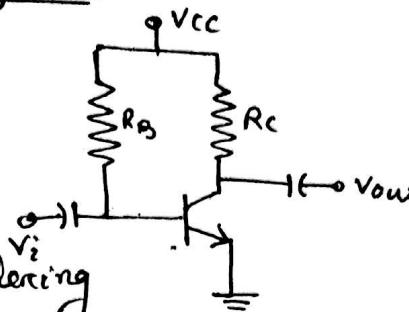

(Fixed Biased Ckt)

Redrawing Input loop

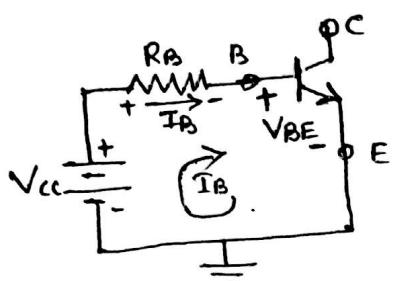


Applying KVL

$$V_{CC} - I_B R_B - V_{BE} = 0$$

Hence $V_{BE} = 0.7V$ for Si
 $= 0.3V$ for Ge

Redrawing Output loop

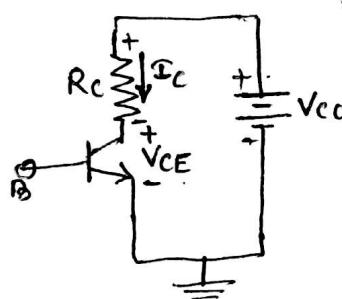

Applying KVL

$$V_{CC} - I_C R_C - V_{CE} = 0$$

V_B is the voltage from Base to Ground.

V_C is the voltage from Collector to Ground.


V_E is the voltage from Emitter to Ground.

$$V_{CE} = V_C - V_E$$

$$\Rightarrow V_{CE} = V_C \quad (\because V_E = 0 \text{ in fixed bias})$$

$$V_{BE} = V_B - V_E$$
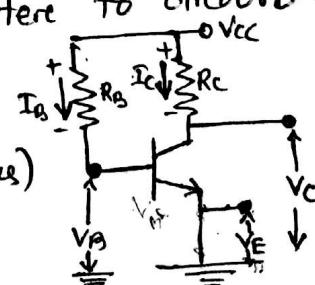
$$\Rightarrow V_{BE} = V_B \quad (\because V_E = 0 \text{ in fixed bias})$$




(10)

(12)

Transistor At Saturation

- Saturation indicates maximum.
- So for a particular design if ~~the~~ maximum current & maximum voltage appear at Transistor then called as transistor is at saturation.

in a fixed biased ckt.

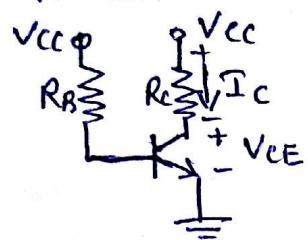


if $V_{CE} = 0$ then the I_c is called I_{Csat} or I_{cmax}

$$o/p \text{ loop} \rightarrow V_{CC} - I_c R_C - V_{CE} = 0$$


if $V_{CE} = 0$
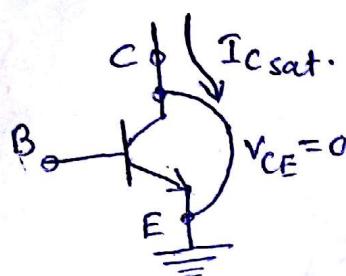
$$\text{then } I_{Csat} = \frac{V_{CC}}{R_C}$$



if $I_c = 0$

$$V_{CE_{\text{sat}}} = V_{CC}$$

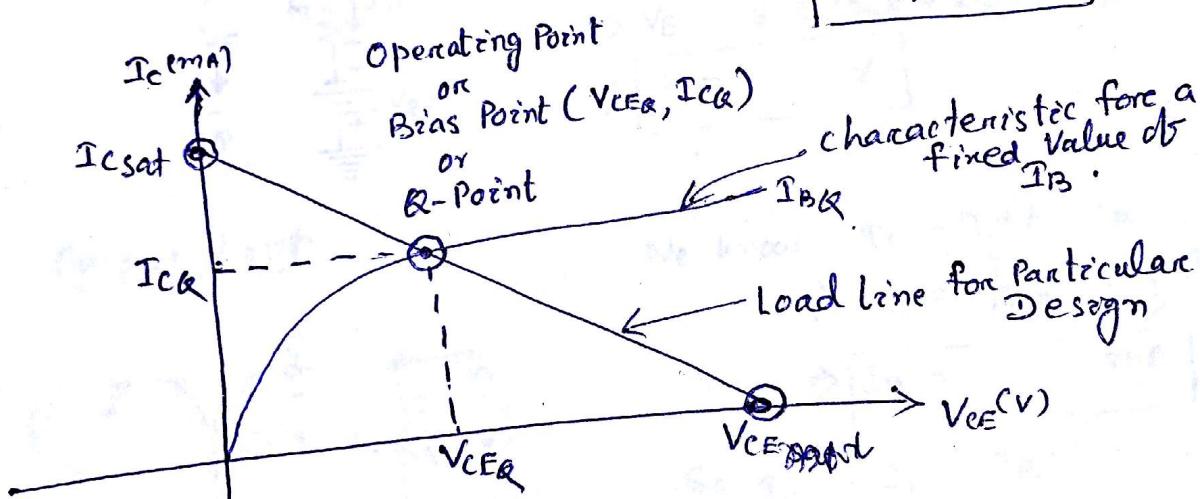


Note So Q-point indicates the operating -

Collector Current I_{CQ}

Base Current I_{BQ}

Collector Emitter Voltage V_{CEQ} .

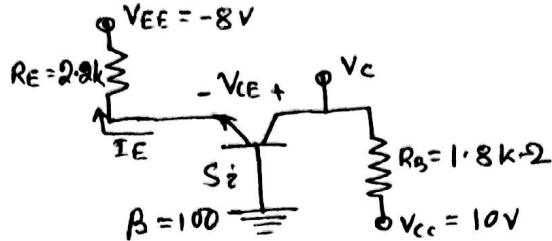(B) For the ckt. shown, determine I_E , V_C , V_E , I_B , V_{CB} , I_C .




Ans

Input Loop

Assuming $V_{BE} = 0.7V$


Applying KVL

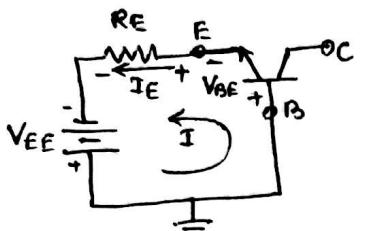

$$V_{EE} - V_{BE} - I_E R_E = 0$$

$$\Rightarrow I_E = \frac{V_{EE} - V_{BE}}{R_E} = \frac{8V - 0.7V}{2.2k} =$$

$$\boxed{I_E = 3.3182 \text{ mA}}$$

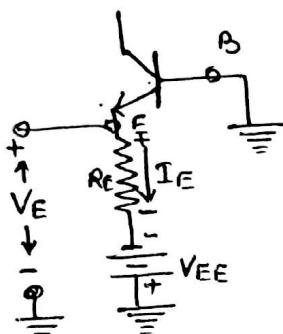


$$V_E - I_E R_E + V_{EE} = 0$$

$$\Rightarrow V_E = 3.3182 \text{ mA} * 2.2k\Omega + 8V =$$

$$\boxed{V_E = 10V}$$

Output Loop

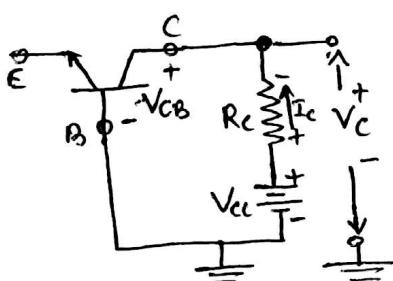

$$\text{We know } I_E = (1 + \beta) I_B$$

$$\Rightarrow I_B = \frac{I_E}{1 + \beta} = \frac{3.3182 \text{ mA}}{101} =$$

$$\boxed{I_B = 33 \mu\text{A}}$$

$$\text{So } I_C = I_E - I_B$$

$$\Rightarrow I_C = 3.3182 \text{ mA} - 33 \mu\text{A}$$

$$\boxed{I_C = 3.285 \text{ mA}}$$

Applying KVL

$$V_{CC} - I_C R_C - V_{CB} = 0$$

$$\Rightarrow V_{CB} = V_{CC} - I_C R_C = 10V - 3.285 \text{ mA} * 1.8k\Omega =$$

$$\boxed{V_{CB} = 4.2 \text{ V}}$$


$$V_C + I_C R_C - V_{CC} = 0$$

$$\Rightarrow V_C = V_{CC} - I_C R_C = 10V - 3.285 \text{ mA} * 1.8k\Omega =$$

$$\boxed{V_C = 4.2 \text{ V}}$$

⑫


(Q) Calculate I_B , I_C , I_E & V_{CE}

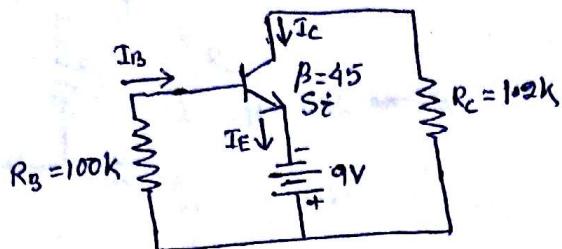

(Q) What do you understand by Q-point? What is its significance?


(Q) Why biasing is necessary in BJT amplifiers?

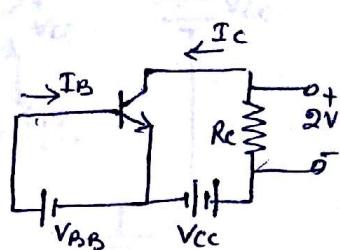(Q) For a transistor $\beta_{FE} = 100$ and voltage drop across R_C is 2 Volts. Find the Base current.



(Q) What is α_{dc} & β_{dc} of a transistor. For a transistor the base current is 100μA and collector current is 2.9mA. Find α_{dc} & β_{dc} .

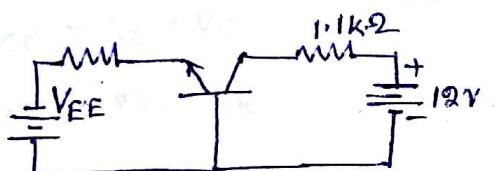(Q) On the ckt find I_C when $V_{CB} = 8V$ and V_{CB} when $I_C = 2mA$.





$$\text{Ans} = I_C = 3.636 \text{ mA}$$

$$\text{Ans} = V_{CB} = 9.8 \text{ V}$$

(Q) For the transistor the $\beta_{dc} = 120$. Calculate the value of R_B that will just saturate the transistor.

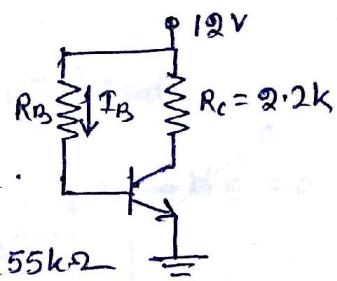Assume $V_{CESat} = 0.3V$ $\text{Ans } R_B = 255k\Omega$



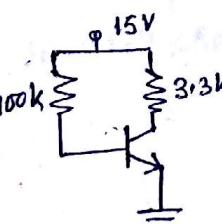
(Q)  (a) Find V_{CE} when $I_C = 1\text{mA}$
(b) Find I_C when $V_{CE} = 10V$
(c) Find V_{CE} when $I_C = 0$

$$\text{Ans } V_{CE} = 11.7V$$

$$\text{Ans } I_C = 1.5mA$$

$$\text{Ans } V_{CE} = 15V$$

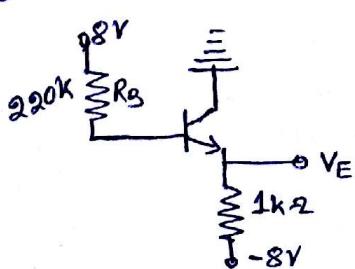(Q) Determine I_E , V_E & V_{CE} for the given ckt.




$$\text{Ans } I_E = 4.81mA$$

$$V_E = -3.186V$$


$$V_{CE} = 3.186V$$

Emitter Stabilized Biasing

(15)

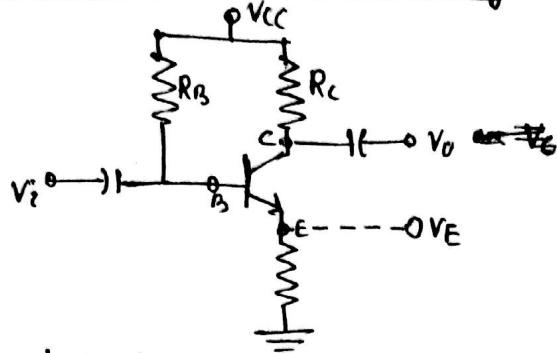

Input Loop

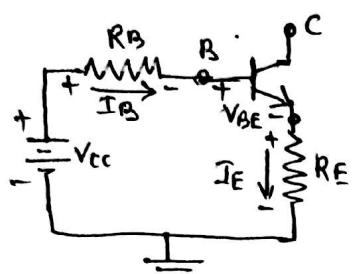

Applying KVL

$$V_{cc} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$\Rightarrow V_{cc} - I_B R_B - V_{BE} - (1+\beta) I_B R_E = 0$$


$$\Rightarrow I_B = \frac{V_{cc} - V_{BE}}{R_B + (1+\beta) R_E}$$

$$V_{CE} = V_C - V_E$$

$$V_{BE} = V_B - V_E$$

At Saturation

Hence

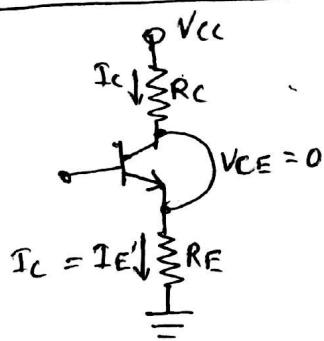

$$I_C = I_E = I_{C_{max}} = I_{C_{sat}}$$


$$\text{Put } V_{CE} = 0 \\ V_{cc} - I_C R_C - I_C R_E - V_{CE} = 0$$

$$\Rightarrow I_{C_{sat}} = \frac{V_{cc}}{R_C + R_E}$$

$$\text{Put } I_C = 0 \\ V_{cc} - I_C R_C - V_{CE} - I_C R_E = 0$$

$$\Rightarrow V_{CE_{sat}} = V_{cc}$$

O/p Loop

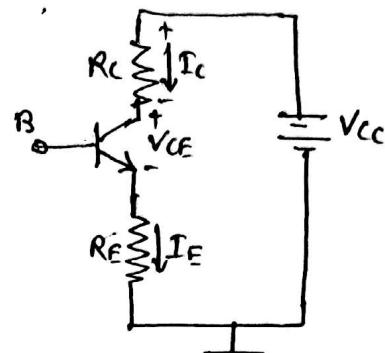

Applying KVL

$$V_{cc} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\Rightarrow V_{CE} = V_{cc} - I_C R_C - I_E R_E$$

$$\Rightarrow V_{CE} = V_C - V_E$$

$$\left[\begin{array}{l} V_E = I_E R_E \\ V_C = V_{cc} - I_C R_C \end{array} \right]$$

(14)