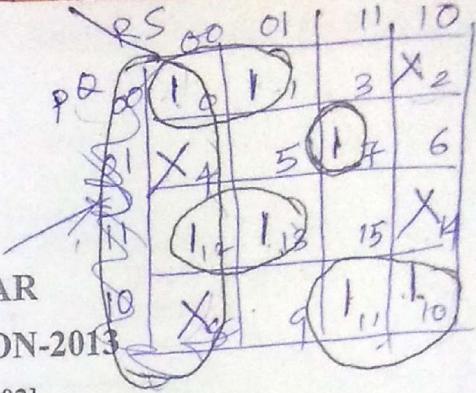


KIIT UNIVERSITY, BHUBANESWAR  
SPRING MID SEMESTER EXAMINATION-2013  
DIGITAL ELECTRONICS CIRCUITS [EC- 402]



Full Marks: 25

Duration: 2Hrs

*Answer any FIVE questions including question No.1 which is compulsory.*


*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable and all parts of a question should be answered at one place only.*

$$\begin{aligned} & \overline{RS} + P\overline{QR} + \\ & P\overline{QR} + P\overline{QR} + \\ & + \overline{PQRS}. \end{aligned}$$

- (1) a) "Gray codes are cyclic but not sequential & self-complementing." Justify. [1x5]  
 b) Perform following arithmetic: (i) BCD addition (749+858),  
 (ii) (-9) - (-6) using 2's complement method.  
 c) Show that,  $U\bar{V} + U\bar{W} + V\bar{W} = U + V\bar{W}$  where U, V and W are Boolean variables.  
 d) Define 'Positive logic system' and 'Negative logic system'.  
 e) Why the row and column values of the K-map are ordered in Gray code rather than binary numerical order, explain in brief.
- (2) Obtain the minimized expression for the following 4-variable Boolean expression using K-map method and implement the minimized expression using minimum numbers of universal gates. [5]  
 $F(P,Q,R,S) = \sum m(0,1,7,10,11,12,13) + d(2,4,8,14)$
- (3) a) Design 4-bit combined adder/subtractor circuit using full adders & XNOR gates only and explain [4] the working in brief.  
 b) Define Reflective codes and explain with proper example in brief. *Gray codes.* [1]

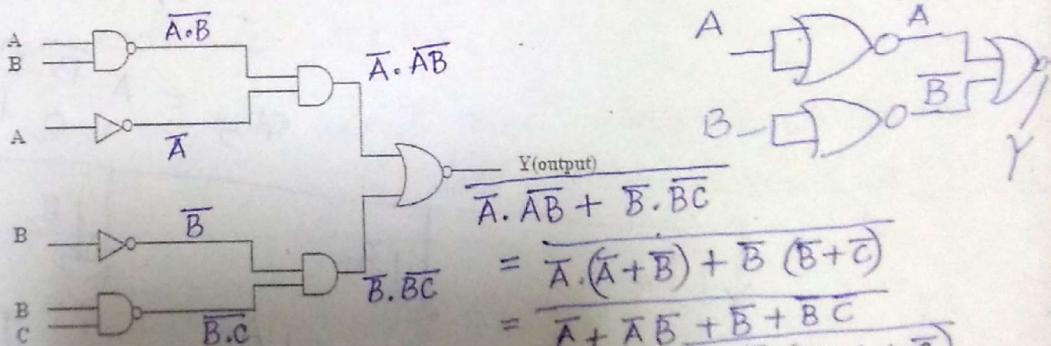- (4) a) Simplify the given logic circuit and implement the simplified expression using only NOR gates. [4]




- b) What is the disadvantage of Ripple carry adder and how can it be minimized? [1]

$$= \overline{A} + \overline{B} (\overline{A} + \overline{B}) [1]$$

- (5) a) What is Decoder? Draw the circuit diagram and truth table of 2-4 decoder having active-LOW output terminals. [2]

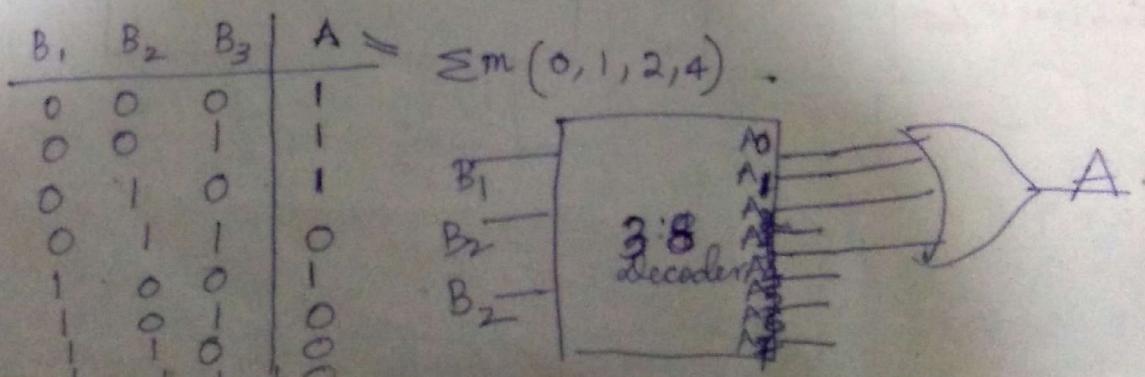- b) In a room there are three electric lamps. For sufficient light intensity, at least two lamps must be ON at the same time. Design a circuit, using 3-8 decoder (having active HIGH output lines) and basic logic gates, which enables an alarm when light intensity in the room is not sufficient. [3]



[4]

(6) a) In the figure given below X, Y and Z are 7-bit Hamming codes. A, B and C are 4-bit data.

where X: 1010011

Y: 1100101


1010011  
P<sub>1</sub>P<sub>2</sub>D<sub>3</sub>P<sub>4</sub>D<sub>5</sub>D<sub>6</sub>D<sub>7</sub>

1101 → C<sub>1</sub> = 1

0111 → C<sub>2</sub> = 1

0011 → C<sub>3</sub> = 0

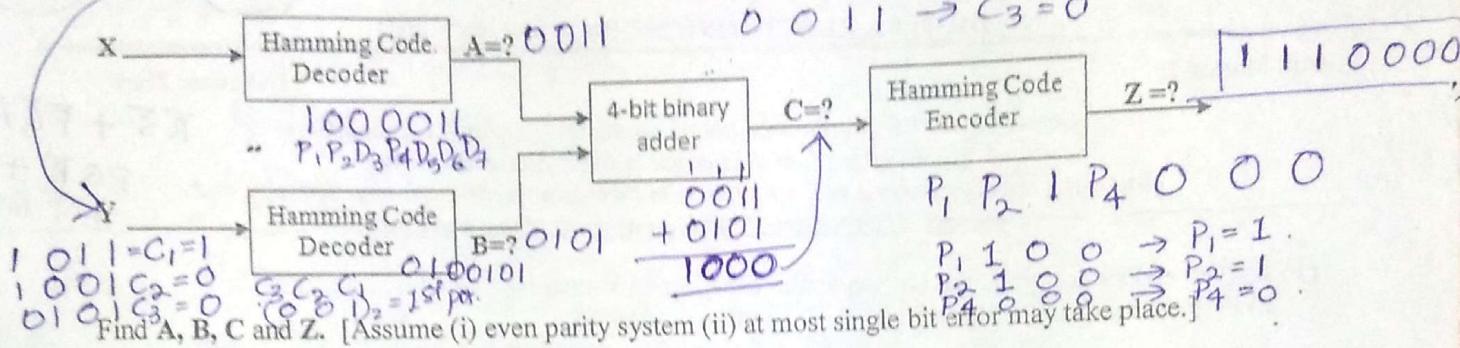C<sub>3</sub>C<sub>2</sub>C<sub>1</sub>  
(0 1 D<sub>2</sub>) = 3<sup>rd</sup> par.



b) Define 'minterm' and 'maxterm' and show that  $m_i = \overline{M_i}$ ,

[1]

(where  $m_i$ :  $i^{\text{th}}$  minterm &  $M_i$ :  $i^{\text{th}}$  maxterm)


$$\text{m}_5 = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

$$M_5 = \overline{A} + B + \overline{C}$$

$$\overline{M_i} = \overline{\overline{A} + B + \overline{C}}$$

$$= \overline{\overline{A}} \cdot \overline{B} \cdot \overline{\overline{C}}$$

$$m_5 = A \cdot \overline{B} \cdot C$$

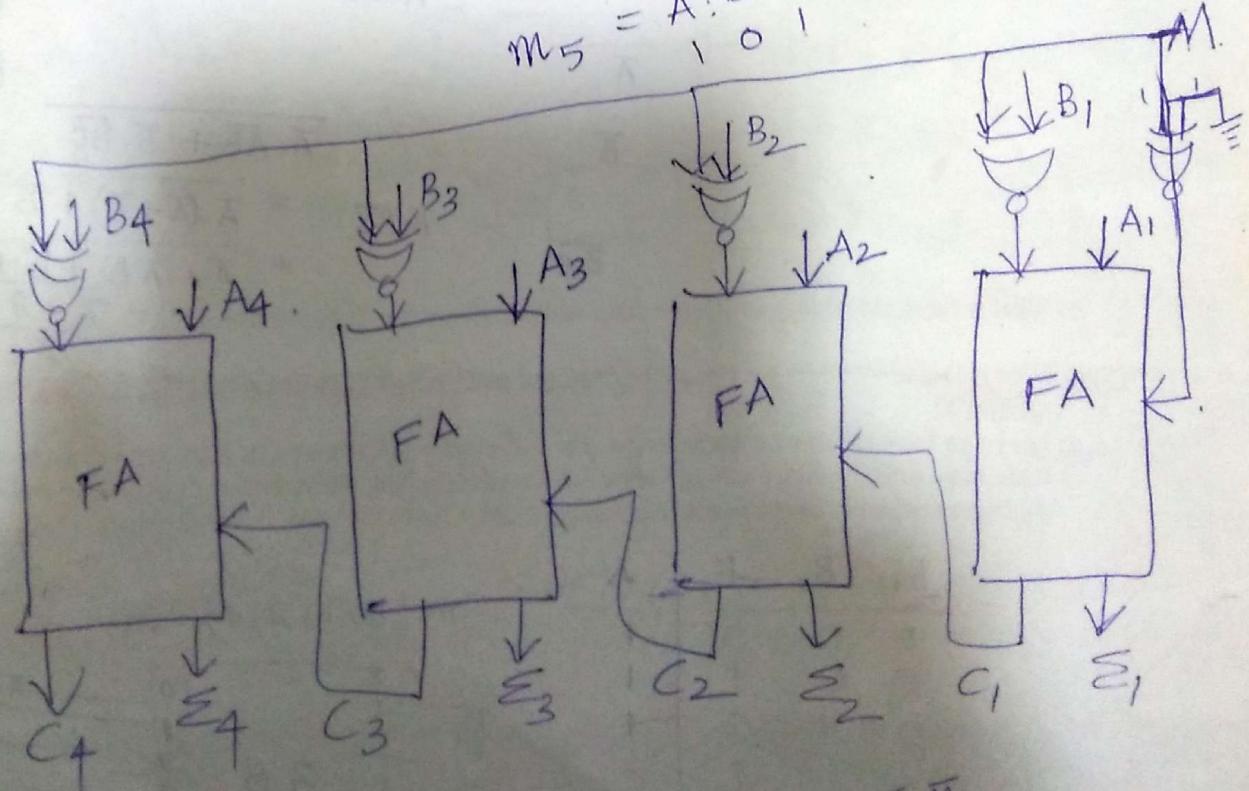

(Q1)

(a) Gray codes are cyclic because two adjacent code words have unit distance b/w them.

ex.  $2 \rightarrow 001\overset{1}{1}$  (only 1 bit change b/w adjacent codewords)  
 $3 \rightarrow 001\overset{1}{0}$

bit width

They are not sequential because we can't always get the succeeding code word by adding binary 1 to preceding code word. e.g.  $11 \rightarrow 1110$  (gray)  
 $12 \rightarrow 1010$  (gray)

They are not self-complementing because we can't get the code word for  $9-N$  by just complementing ( $1's$  complement) the code word for  $N$ .

e.g.  $4 = 0110$  (gray)  
 $\downarrow 1's \text{ complement}$

$(9-4)=5 \neq 1001$  (gray)

For 5, gray code is 0111.

$\therefore$  "Gray codes are cyclic but not sequential & self-complementing."

(b)  $749 + 858$

$749 \rightarrow (0111, 0100, 1001)_{8421}$

$858 \rightarrow (1000, 0101, 1000)_{8421}$

$$\begin{array}{r}
 \hline
 1111, 1010, 0001 \\
 + 0110, 0110, 0110 \\
 \hline
 1,0110, 0000, 0111
 \end{array}$$

(Invalid BCD &  
 Add 0110 to each nibble.  
 $\therefore 749 + 858 = 1607$ )

1 .. 6      0      7

$$(b) \text{iii) } (-9) - (-6)$$

$$= -9 + 6 = 6 + (-9) = 6 + (\text{2's complement of } 9)$$

$$(+9) = 00001001$$

$$(-9) = \text{2's complement of } (+9) = 11110111$$

$$(+6) = 00000110$$

$$\begin{array}{r} \therefore 00000110 \\ + 11110111 \\ \hline \underbrace{11111101}_{\therefore (-3)} \end{array}$$

(no carry).

The result is -ve. (MSB bit = 1)  
and is in 2's complement form.

$\therefore$  True result =

2's complement of (2's complement form of result)

$$= 00000011 = (+3)$$

$$(c) U\bar{V} + UW + V\bar{W} = U + V\bar{W}$$

Applying Consensus theorem in 1st & 3rd term,  
we get additional  $U\bar{W}$ ,

LHS =

$$\Rightarrow U\bar{V} + UW + V\bar{W} + U\bar{W}$$

$$= U\bar{V} + UW + U\bar{W} + V\bar{W}$$

$$= U\bar{V} + U(W + \bar{W}) + V\bar{W} \quad [\because AB + AC = A(B + C)]$$

$$= U\bar{V} + U \cdot 1 + V\bar{W} \quad [\because A + \bar{A} = 1]$$

$$= U(\bar{V} + 1) + V\bar{W} \quad [\because A + 1 = 1].$$

$$= U + V\bar{W} = RHS$$

Date 16/9

(b)

Positive Logic System

If HIGH voltage level is used to represent 1 and LOW voltage level

to represent 0, the system is called positive logic system.

Negative Logic System →

If HIGH voltage level is used to represent 0 and LOW voltage level is used to represent 1, the system is called negative logic system.

(c) Row and column values of K-map are ordered in Gray codes rather than binary because Gray codes are unit distance codes (there is change in one bit position only b/w adjacent code words).

(Q2)

| PQ \ RS | 00   | 01   | 11  | 10   |
|---------|------|------|-----|------|
| 00      | 1 0  | 1 1  | 1 3 | X 2  |
| 01      | X 4  |      | 1 5 | 1 6  |
| 11      | 1 12 | 1 13 |     | X 15 |
| 10      | X 8  |      | 1 9 | 1 10 |

$$F(P, Q, R, S) = \overline{P} \overline{Q} \overline{R} + P \overline{Q} \overline{R} + P \overline{Q} R + \overline{P} Q R S.$$

Using NAND



$$\begin{aligned} F &= \overline{\overline{P} \overline{Q} \overline{R}} + \overline{P} \overline{Q} \overline{R} + \overline{P} \overline{Q} R + \overline{\overline{P} Q R S} \\ &= \overline{\overline{P} \overline{Q} \overline{R}} \cdot \overline{P} \overline{Q} \overline{R} \cdot \overline{P} \overline{Q} R \cdot \overline{\overline{P} Q R S} \end{aligned}$$

Using NOR


$$\begin{aligned} F &= \overline{P} \overline{Q} \overline{R} + \overline{P} \overline{Q} R + \overline{P} Q \overline{R} + \\ &\quad \overline{\overline{P} Q R S} \end{aligned}$$

$$\begin{aligned} &= P + Q + R + \overline{P} + \overline{Q} + \overline{R} + \overline{P} \overline{Q} + \overline{R} \\ &\quad + P + \overline{Q} + \overline{R} + S \end{aligned}$$

(no. of gates = 8) ✓  
(Ans)

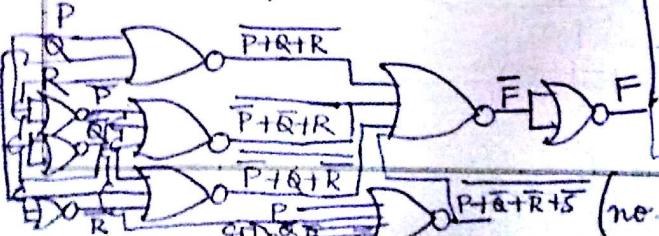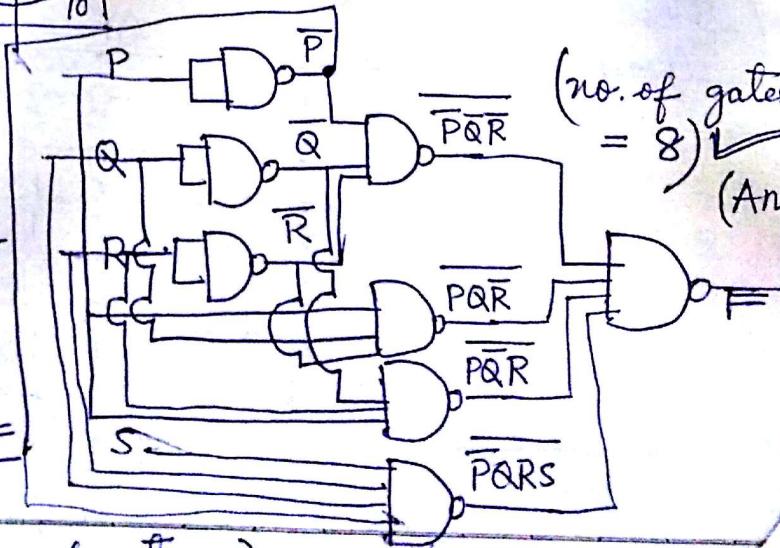

(no. of gates = 10)

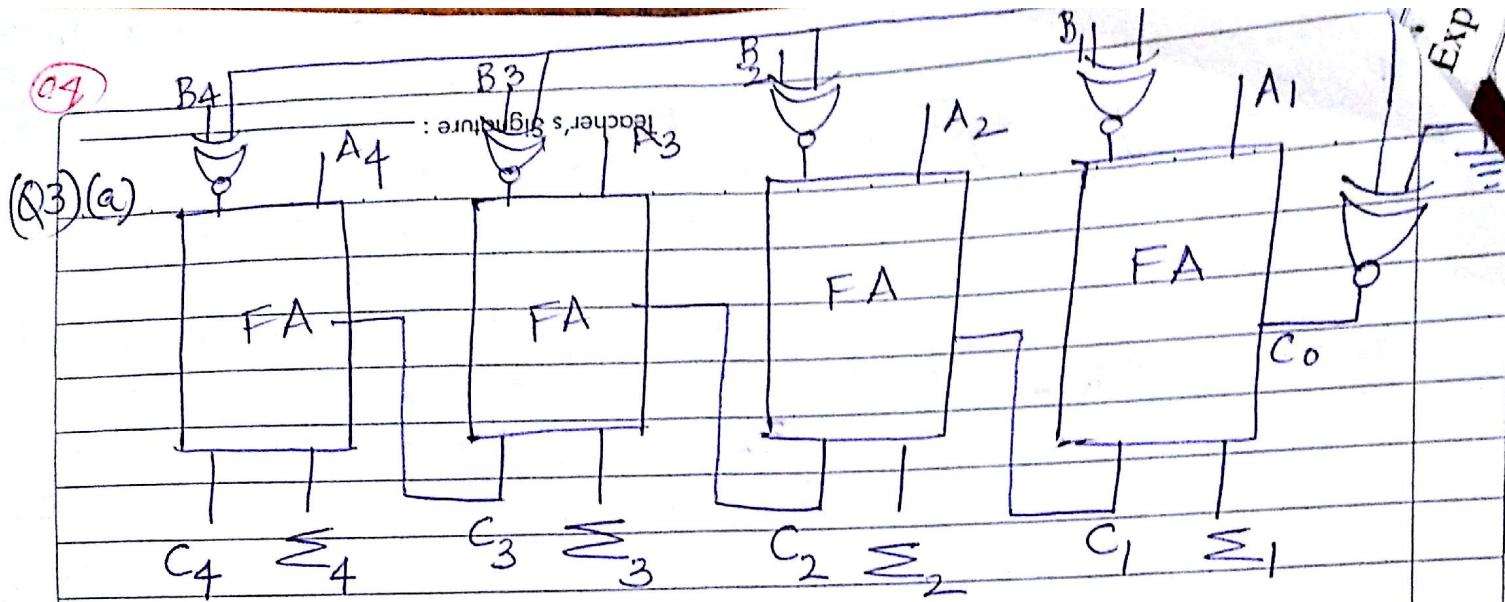

XNOR gate

If  $M=0$ , subtractor.

$$M \odot B$$

$$= MB + \overline{M} \overline{B}$$

(2's complement

method of

subtraction)

$$= 0 \cdot B + \overline{0} \cdot \overline{B}$$

$$= \overline{B}$$

If  $M=1$ , adder.

$$M \odot B$$

$$= MB + \overline{M} \overline{B}$$

$$= 1 \cdot B + T \cdot \overline{B}$$

$$= B.$$

(b) Reflective codes are those in which the 'n' LSB bits of the code words  $2^n$  through  $2^{n+1}-1$  are the mirror images of the code words 0 through  $2^n$ .

e.g. Gray codes.

Decimal      Gray code

0      0 0 0 0

1      0 0 0 1

2      0 0 1 1

3      0 0 1 0

4      0 1 1 0

5      0 1 1 1

6      0 1 0 1

7      0 1 0 0

8      1 1 0 0

9      1 1 0 1

10     1 1 1 1

11     1 1 1 0

12     1 0 1 1

13     1 0 1 0

14     1 0 0 1


15     1 0 0 0

mirror

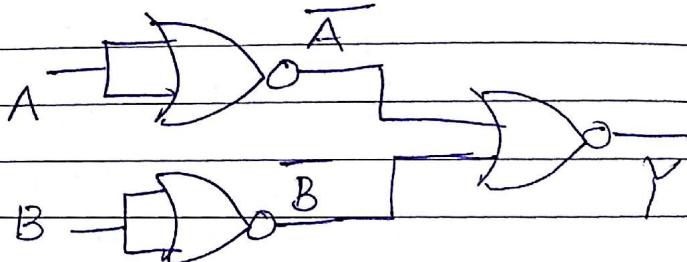Q4) (a)  $Y = A \cdot B$  after simplification using De-Morgan's law

Using NOR.

$$Y = \overline{A \cdot B} = \overline{\overline{A} + \overline{B}}$$



(b) → Carry Propagation Delay.


→ Using Look-Ahead Carry adder.

Q5) (a) Book. (given)

(b)

| $L_1$ | $L_2$ | $L_3$ | Alarm |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 1     |
| 0     | 0     | 1     | 1     |
| 0     | 1     | 0     | 1     |
| 0     | 1     | 1     | 0     |
| 1     | 0     | 0     | 1     |
| 1     | 0     | 1     | 0     |
| 1     | 1     | 0     | 0     |
| 1     | 1     | 1     | 0     |
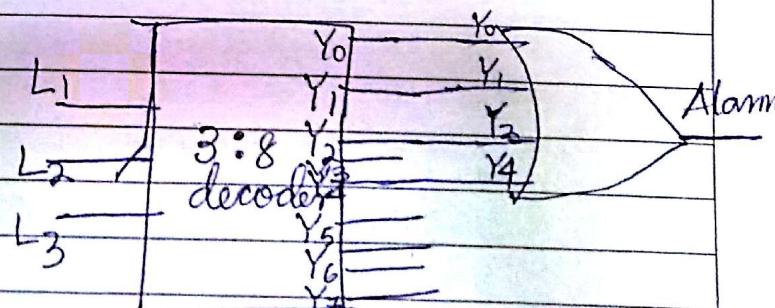
$$\therefore \text{Alarm} = \sum m(0, 1, 2, 4).$$



Teacher's Signature : \_\_\_\_\_

